Summary Modeling and Simulation of Complex Power Systems WS 2013/14<sup>1</sup> Version: 8. April 2014

# 1 Natural Coupling

- circuit composed of b branches and n nodes
- calculation of 2b unknowns (voltage and current of each branch)

explicit variable: known, e.g. x = 2

implicit variable: unknown, to calculate, e.g.  $x^2 = 2^x$ 

# 1.1 Nodal Analysis (NA)

- one node («0») as reference potential (known)
- voltage of each of n-1 nodes  $\vec{x}$  to calculate
- n-1 equations to solve
- best option for circuit simulation
- information of electronic circuit fully contained in voltage
- $\mathbf{G} \cdot \vec{x} = \vec{s}$  with nodal conductance matrix  $\mathbf{G}$  and current injection vector  $\vec{s}$

### 1.1.1 by inspection

build nodal conductance matrix  $\mathbf{G}$  and current injection vector  $\vec{s}$  from node equations

### 1.1.2 matrix stamp

T

k

construction of the nodal conductance matrix  $\mathbf{G}$  and current injection vector  $\vec{s}$  by components

### resistance R between nodes i and j:

$$\begin{array}{c} R & i & j \\ i & & & \\ \leftarrow & & \\ e_i - e_j \end{array} \qquad \mathbf{G}_{sub} = \frac{i}{j} \begin{bmatrix} \frac{1}{R} & \frac{-1}{R} \\ \frac{-1}{R} & \frac{1}{R} \end{bmatrix}$$

ideal current source I between nodes i and j: (injecting in node i)

$$j \circ - \circ i \qquad \vec{s}_{sub} = \stackrel{i}{\underset{j}{\overset{I}{\begin{bmatrix}} I \\ -I \end{bmatrix}}}$$

real voltage source V with in series resistance R between nodes i and j: (with + at node i)

$$j \circ \underbrace{V}_{V} \xrightarrow{R} \circ i \qquad \mathbf{G}_{sub} = \begin{bmatrix} i & j \\ \frac{1}{R} & \frac{-1}{R} \\ \frac{-1}{R} & \frac{1}{R} \end{bmatrix} \text{ and } \vec{s}_{sub} = \begin{bmatrix} i \\ \frac{V}{R} \\ -\frac{V}{R} \end{bmatrix}$$

### 1.2 Modified Nodal Analysis (MNA)

- extension of NA for modeling ideal voltage sources
- important to represent real devices like controlled power supplies
- add one equation (voltage between nodes) and one unknown (current through the ideal voltage source)
- nodal conductance matrix **G** with  $(n 1 + v_{ideal}) \times (n 1 + v_{ideal})$
- source vector  $\vec{s}$  with  $(n 1 + v_{ideal}) \times 1$
- voltage of nodes and currents of ideal voltage sources  $\vec{x}$  to calculate
- apply matrix stamp for every ideal voltage source

### ideal voltage source $V_{kl}$ between nodes k and l:

$$V_{kl} \uparrow \stackrel{\circ}{\stackrel{+}{\stackrel{-}{\rightarrow}}} V_{kl} \qquad \begin{array}{c} k & l \\ 0 & 0 & | & 1 \\ 0 & 0 & | & -1 \\ \hline 1 & -1 & | & 0 \end{array} \right], \ \vec{x}_{sub} = l \left[ \begin{array}{c} 0 \\ 0 \\ \hline I_{kl} \end{array} \right] \text{ and } \vec{s}_{sub} = l \left[ \begin{array}{c} 0 \\ 0 \\ \hline V_{kl} \end{array} \right]$$

<sup>&</sup>lt;sup>1</sup>please report errors to robert.uhl@rwth-aachen.de

#### 1.3Solution methods

- Gaussian elimination: solution  $\vec{x}$  by processing **G** and  $\vec{s}$
- LU factorization: useful for multiple solutions with fixed G and changing  $\vec{s}$  (see resistive companion)

#### 1.4**Controlled** sources

- 4 terminal device
- 2 terminals for controlling variable
- 2 terminals for controlled variable

#### examples:

- small signal representation of transistors
- operational amplifiers
- ideal transformers

#### Voltage Controlled Current Source (VCCS) 1.4.1

- directly representable in nodal analysis
- characteristic equation:  $I_{pq} = g \cdot V_{mn}$  with trans-conductance g and  $V_{mn} = V_m V_n$ •



#### Voltage Controlled Voltage Source (VCVS) 1.4.2

- not directly representable in nodal analysis
- characteristic equation:  $V_{pq} = \alpha \cdot V_{mn}$  with  $V_{pq} = V_p V_q$  and  $V_{mn} = V_m V_n$ •



#### for nodal analysis:

- 1. matrix stamp for VCCS with gain  $g = \frac{-\alpha}{R_{int}}$ 2. matrix stamp for parallel small internal resistance  $R_{int}$  between nodes p and q

#### matrix stamp for modified nodal analysis:

$$\mathbf{G}_{sub} = \begin{bmatrix} m & n & p & q \\ n & & & 0 \\ p & & & 0 \\ q & & & 1 \\ \hline -\alpha & \alpha & 1 & -1 & 0 \end{bmatrix} \text{ and } \vec{x}_{sub} = \begin{bmatrix} -1 \\ \hline I_{pq} \end{bmatrix}$$

#### Current Controlled Current Source (CCCS) 1.4.3

- not directly representable in nodal analysis
- characteristic equation:  $I_{pq} = \beta \cdot I_{mn}$ •



#### for nodal analysis:

- 1. matrix stamp for VCCS with gain  $g = \frac{\beta}{R_{mn}}$ 2. matrix stamp for small resistance  $R_{mn}$  between nodes m and n

#### matrix stamp for modified nodal analysis:

$$\mathbf{G}_{sub} = \begin{bmatrix} m & n & p & q \\ n \\ n \\ q \\ q \end{bmatrix} \begin{bmatrix} m & n & p & q \\ & & & 1 \\ & & & -1 \\ & & & \beta \\ \hline 1 & -1 & 0 & 0 & 0 \end{bmatrix} \text{ and } \vec{x}_{sub} = \begin{bmatrix} \\ \hline I_{mn} \end{bmatrix}$$

### 1.4.4 Current Controlled Voltage Source (CCVS)

- not directly representable in nodal analysis
- characteristic equation:  $V_{pq} = r \cdot I_{mn}$  with  $V_{pq} = V_p V_q$



### for nodal analysis:

- 1. matrix stamp for VCCS with gain  $g = \frac{\beta}{R_{mn} \cdot R_{int}}$ 2. matrix stamp for small resistance  $R_{mn}$  between nodes m and n3. matrix stamp for small resistance  $R_{int}$  between nodes p and q

### matrix stamp for modified nodal analysis:

$$\mathbf{G}_{sub} = \begin{array}{ccccc} m & n & p & q \\ m & & 1 & 0 \\ n \\ q \\ q \\ \hline 1 & -1 & 0 & 0 \\ 0 & 0 & 1 & -1 \\ \hline 1 & -1 & 0 & 0 & 0 \\ 0 & 0 & 1 & -1 \\ \hline -r & 0 \\ \end{array} \right] \text{ and } \vec{x}_{sub} = \begin{bmatrix} \hline I_{mn} \\ I_{pq} \\ \end{bmatrix}$$

#### Linear circuits transient analysis - Resistive companion 2

- transformation of dynamic elements in a corresponding DC equivalent circuit
- represents an iteration of an integration method

#### 2.1Integration methods

- integration time step  $\Delta t$
- smaller time step is more accurate/better
- explicit method:
  - predict the future value of the solution by using information from the previous steps
  - may diverge for large time step
  - faster calculation
- implicit method
  - requires knowledge of a value at the future time step
  - always numerically stable/will always converge
  - more effort for calculation

#### 2.1.1Euler Forward (EF)

- assumes function x(t) is constant between  $k \cdot \Delta t$  and  $(k+1) \cdot \Delta t$  and equal to value  $x(k \cdot \Delta t)$
- result:  $y(k+1) = y(k) + x(k) \cdot \Delta t$
- explicit method

#### 2.1.2Euler Backward (EB)

- assumes function x(t) is constant between  $k \cdot \Delta t$  and  $(k+1) \cdot \Delta t$  and equal to value  $x((k+1) \cdot \Delta t)$
- result:  $y(k+1) = y(k) + x(k+1) \cdot \Delta t$
- implicit method

#### 2.1.3Trapezoidal Rule (TR)

- assumes function x(t) is linear between  $k \cdot \Delta t$  and  $(k+1) \cdot \Delta t$  with values  $x(k \cdot \Delta t)$  and  $x((k+1) \cdot \Delta t)$
- result:  $y(k+1) = y(k) + \frac{x(k) + x(k+1)}{2} \cdot \Delta t$
- implicit method
- combination of Euler Forward and Euler Backward for better accuracy

#### 2.2Resistive companion formulation for an inductance



- Euler Forward:  $i(k+1) = i(k) + \frac{\Delta t}{L} \cdot v(k) = I_L(k) + 0 \cdot v(k+1)$  (ideal current source) Euler Backward:  $i(k+1) = i(k) + \frac{\Delta t}{L} \cdot v(k+1) = I_L(k) + G_L \cdot v(k+1)$  Trapezoidal Rule:  $i(k+1) = \frac{\Delta t}{2L} \cdot v(k+1) + (i(k) + \frac{\Delta t}{2L} \cdot v(k)) = G_L \cdot v(k+1) + I_L(k)$ with  $G_L = \frac{\Delta t}{2L}$  and  $I_L(k) = i(k) + G_L \cdot v(k)$

#### $\mathbf{2.3}$ Resistive companion formulation for a capacitance



- Euler Forward:  $v(k+1) = v(k) + \frac{\Delta t}{C} \cdot i(k)$ (ideal voltage source)
- Euler Backward:  $v(k+1) = v(k) + \frac{\Delta t}{C} \cdot i(k)$  (ited voltage bolice) Euler Backward:  $v(k+1) = v(k) + \frac{\Delta t}{C} \cdot i(k+1)$   $\iff i(k+1) = \frac{C}{\Delta t} \cdot v(k+1) \frac{C}{\Delta t} \cdot v(k) = G_C \cdot v(k+1) I_C(k)$  Trapezoidal Rule:  $v(k+1) = v(k) + \frac{\Delta t}{2C} \cdot (i(k+1) + i(k))$   $\iff i(k+1) = \frac{2C}{\Delta t} \cdot v(k+1) (i(k) + \frac{2C}{\Delta t} \cdot v(k)) = G_C \cdot v(k+1) I_C(k)$ with  $G_C = \frac{2C}{\Delta t}$  and  $I_C(k) = i(k) + G_C \cdot v(k)$

# 3 Signal Coupling

## 3.1 State space

### system state:

Amount of information at any time  $t_0$  that, together with all inputs for  $t \ge t_0$ , uniquely determines the behaviour of the system for all  $t \ge t_0$ . State variables must be continuous and linearly representable.

### state equations:

 $\dot{\vec{x}}(t) = \vec{f}(\vec{x}, \vec{u}, t)$  explicit first order differential equations

### output equations:

 $\vec{y}(t)=\vec{g}(\vec{x},\vec{u},t)$ 

### linear time-invariant system:

 $\dot{\vec{x}}(t) = \mathbf{A} \cdot \vec{x}(t) + \mathbf{B} \cdot \vec{u}(t)$  $\vec{y}(t) = \mathbf{C} \cdot \vec{x}(t) + \mathbf{D} \cdot \vec{u}(t)$ 

### 3.2 Integration method - Predictor and corrector

improves accuracy compared with Euler-Forward or Euler-Backward

 $\dot{x} = f(x, t)$  $t_k \to t_{k+1}$ 

**predictor:** (like Euler Forward)  $\hat{x}_{k+1} = x_k + dy_1 \cdot \Delta t$  with  $dy_1 = f(x_k, t_k)$  **corrector:** (like Trapezoidal Rule)  $x_{k+1} = x_k + \frac{dy_1 + dy_2}{2} \cdot \Delta t$  with  $dy_2 = f(\hat{x}_{k+1}, t_{k+1})$ 

### 3.3 Automatic state equations for circuits

- combines signal coupling and natural coupling
- uses branch parameters and circuit topology (natural coupling)
- automatically generates state space model (signal coupling)
- numerical integration technique can be selected after formulation, which simplifies programming of variable time-step integration techniques
- simple development and implementation of simulation

#### node incidence matrix $\mathbf{A}_a$ : $((n) \times (b))$

- each row corresponds to a node (n)
- each column corresponds to a branch (b) and contains two non-zero elements (1 and -1)
- for positive terminal of branch *j* connected to node *i*,  $a_{ij} = 1$
- for negative terminal of branch j connected to node i,  $a_{ij} = -1$
- $\mathbf{A}_a \cdot \vec{\imath}_{br} = \vec{0}$  with branch currents  $\vec{\imath}_{br}$  (from KCL)

$$\mathbf{A}_a \stackrel{\scriptscriptstyle\frown}{=} \tilde{\mathbf{A}}_a = \quad \begin{bmatrix} \mathbf{I}_{(n-1)\times(n-1)} & \hat{\mathbf{A}}_{(n-1)\times(b-n+1)} \\ \mathbf{0}_{(1)\times(n-1)} & \mathbf{0}_{(1)\times(b-n+1)} \end{bmatrix} \qquad (by \ matrix$$

(by matrix operations)

**basic loop matrix B**<sub>b</sub>:  $((b - n + 1) \times (b))$ 

- each row corresponds to a mesh in the circuit (b n + 1)
- each column corresponds to a branch (b)
- -1 and 1 represents the direction of the branch voltage in the mesh
- $\mathbf{B}_b \cdot \vec{v}_{br} = \vec{0}$  with branch voltages  $\vec{v}_{br}$

• 
$$\mathbf{B}_b^T = \begin{bmatrix} -\hat{\mathbf{A}} \\ \mathbf{I} \end{bmatrix}$$

•  $\vec{i}_{br} = \vec{\mathbf{B}_b^T} \cdot \vec{i}_x$  with independent branch currents  $\vec{i}_x$ 

branch model: (not suitable for representing all systems)



$$v_i = r_i \cdot i_i + L_i \cdot \frac{di_i}{dt} + e_i + P_i \cdot \int (i_i + j_i) dt$$

state variables: (length of single sub-vectors is equal to number of branches)

$$\vec{x} = \begin{bmatrix} \vec{q_c} \\ \vec{\imath_x} \end{bmatrix}$$

input variables:  $\begin{bmatrix} \vec{\eta} \\ \vec{\eta} \end{bmatrix}$ 

$$\vec{u} = \begin{bmatrix} Jbr\\ \vec{e}_{br} \end{bmatrix}$$

output variables:  $\begin{bmatrix} \vec{v}_i \end{bmatrix}$ 

$$\vec{y} = \begin{bmatrix} \imath_{br} \\ \vec{v}_{br} \end{bmatrix}$$

resulting state space matrices:

$$\mathbf{A} = \frac{\dot{q}_c}{\dot{t}_x} \begin{bmatrix} \mathbf{0} & \mathbf{M}^T \cdot \mathbf{B}_b^T \\ -\mathbf{L}_x^{-1} \cdot \mathbf{P}_x & -\mathbf{L}_x^{-1} \cdot (\mathbf{r}_x + \frac{d}{dt}\mathbf{L}_x) \end{bmatrix} \qquad \mathbf{B} = \frac{\dot{q}_c}{\dot{t}_x} \begin{bmatrix} \mathbf{M}^T & \mathbf{0} \\ \mathbf{0} & -\mathbf{L}_x^{-1} \cdot \mathbf{B}_b \end{bmatrix}$$
$$\mathbf{C} = \frac{\vec{v}_{br}}{\vec{v}_{br}} \begin{bmatrix} \mathbf{0} & \mathbf{0} \\ \mathbf{P}_{br} \cdot \mathbf{M} - \mathbf{L}_{br} \cdot \mathbf{B}_b^T \cdot \mathbf{L}_x^{-1} \cdot \mathbf{P}_x & (\mathbf{r}_{br} + \frac{d}{dt}\mathbf{L}_{br}) \cdot \mathbf{B}_b^T - \mathbf{L}_{br} \cdot \mathbf{B}_b^T \cdot \mathbf{L}_x^{-1} \cdot (\mathbf{r}_x + \frac{d}{dt}\mathbf{L}_x) \end{bmatrix}$$
$$\mathbf{D} = \begin{bmatrix} \vec{v}_{br} & \vec{v}_{br} \\ \mathbf{0} & \mathbf{I} - \mathbf{L}_{br} \cdot \mathbf{B}_b^T \cdot \mathbf{L}_x^{-1} \cdot \mathbf{B}_b \end{bmatrix}$$

with:

 $\mathbf{r}_x = \mathbf{B}_b \cdot \mathbf{r}_{br} \cdot \mathbf{B}_b^T$ 

#### $\mathbf{L}_x = \mathbf{B}_b \cdot \mathbf{L}_{br} \cdot \mathbf{B}_b^T$ $\mathbf{L}_x$ has to be invertible! (minimum one branch with L)

$$\mathbf{P}_x = \mathbf{B}_b \cdot \mathbf{P}_{br} \cdot \mathbf{M}$$

**M**:  $m_{ij} = 1$  if capacitor j is in the branch i, else  $m_{ij} = 0$  ((b) × (capacitors))

$$\vec{q}_c = \int \vec{i}_c \, dt \qquad \vec{q}_c = \mathbf{M}^T \cdot \vec{q}_{br}$$

diagonal resistance matrix  $\mathbf{r}_{br}$ : diagonal entries correspond to branch resistances  $r_i$ 

### branch inductance matrix $\mathbf{L}_{br}$ :

- self-inductances  $L_i$  (diagonal entries)
- mutual-inductances  $M_{ij}$  (off-diagonal entries)

branch potential coefficient matrix  $\mathbf{P}_{br}$ : diagonal entries for reciprocal capacitances  $\frac{1}{C_i}$  of corresponding branch *i* 

#### **Diakoptics** 4

- dividing (tearing) the original network into a number of isolated subnetworks
- matrix of coefficients for each small network is inverted independently
- solution of the full network obtained from matrices of subnetworks
- no current or voltage sources in the removed branches, only basic components allowed
- removed branches must not form a closed loop or contain nodes not included in the remaining network
- as many variables as were in the original problem plus as many additional variables as there are removed branches

### advantages:

- reduction of computational effort  $(n^3)$
- reduction of needed storage
- economical
- solution is obtained directly by a number of definite steps without any approximations or iterations

### disadvantages:

- n additional calculations for n removed branches, may overweight the advantages of this method
- decouple the network manually

### notation:

- index  $\alpha$ : nodal quantities
- index  $\beta$ : mesh quantities
- index  $\psi$ : removed branch quantities •

#### 4.1 mesh current analysis

- 1. known voltage sources  $\vec{E}_{\beta}$  in branches
- 2. unknown mesh currents  $\vec{i}_{\beta}$  (to calculate)
- 3. build equivalent network with equivalent voltage sources  $\vec{e}_{\beta}$
- 4. build removed network with equivalent current sources  $\tilde{\vec{i}}_{\psi}$  and voltages across removed branches  $\vec{v}_{\psi}$
- 5. build  $\vec{i}_{\psi}$  from mesh currents  $\vec{i}_{\beta}$ :

 $\tilde{\vec{i}}_{\psi} = \mathbf{C}_{\psi\beta} \cdot \vec{i}_{\beta}$  with connection matrix  $\mathbf{C}_{\psi\beta}$ 

- 6. build  $\vec{e}_{\beta}$  from voltages across removed branches  $\vec{v}_{\psi}$ :
- $\vec{e}_{\beta} = \mathbf{B}_{\beta\psi} \cdot \vec{v}_{\psi} = -\mathbf{C}^t_{\beta\psi} \cdot \vec{v}_{\psi}$
- 7. build mesh current equations of equivalent network:  $\hat{\mathbf{Z}}_{\beta\beta} \cdot \hat{\imath}_{\beta} = \vec{E}_{\beta} + \hat{\vec{e}}_{\beta}$  with block diagonal impedance matrix  $\hat{\mathbf{Z}}_{\beta\beta}$  of divided subnetworks
- 8. build relation between currents and voltages of removed network:

$$ilde{ec{i}}_{\psi} = \mathbf{Y}_{\psi\psi} \cdot ec{v}_{\psi}$$

- 9. build fundamental equations of Diakoptics: 
  $$\begin{split} \tilde{\mathbf{Z}}_{\beta\beta} \cdot \vec{\imath}_{\beta} &= \vec{E}_{\beta} - \mathbf{C}_{\beta\psi}^{t} \cdot \vec{v}_{\psi} \\ \mathbf{Y}_{\psi\psi} \cdot \vec{v}_{\psi} &= \mathbf{C}_{\psi\beta} \cdot \vec{\imath}_{\beta} \end{split}$$
- 10. build solution for unknown mesh currents  $\vec{i}_{\beta}$ :

$$\vec{i}_{\beta} = \tilde{\mathbf{Z}}_{\beta\beta}^{-1} \cdot \left( \vec{E}_{\beta} - \mathbf{C}_{\beta\psi}^{t} \cdot \tilde{\mathbf{Y}}_{\psi\psi}^{-1} \cdot \mathbf{C}_{\psi\beta} \cdot \tilde{\mathbf{Z}}_{\beta\beta}^{-1} \cdot \vec{E}_{\beta} \right)$$
  
with  $\tilde{\mathbf{Y}}_{\psi\psi} = \mathbf{Y}_{\psi\psi} + \mathbf{C}_{\psi\beta} \cdot \tilde{\mathbf{Z}}_{\beta\beta}^{-1} \cdot \mathbf{C}_{\beta\psi}^{t}$ 

#### 4.2nodal voltage analysis

- 1. known current injections  $\vec{I}_{\alpha}$  in nodes
- 2. unknown nodal voltages  $\vec{v}_{\alpha}$  (to calculate)
- 3. build equivalent network with equivalent current sources  $\vec{i}_{\alpha}$
- 4. build removed network with equivalent voltage sources  $\vec{e}_{\psi}$  and currents through removed branches  $\vec{i}_{\psi}$
- 5. build  $\vec{i}_{\alpha}$  from currents through removed branches  $\vec{i}_{\psi}$ :
- $\vec{i}_{\alpha} = \mathbf{C}_{\alpha\psi} \cdot \vec{i}_{\psi}$  with connection matrix  $\mathbf{C}_{\alpha\psi}$
- 6. build  $\vec{e}_{\psi}$  from voltages across removed branches  $\vec{v}_{\alpha}$ :  $\vec{e}_{\psi} = \mathbf{B}_{\psi\alpha} \cdot \vec{v}_{\alpha} = -\mathbf{C}_{\psi\alpha}^t \cdot \vec{v}_{\alpha}$
- 7. build nodal voltage equations of equivalent network:
- $\tilde{\mathbf{Y}}_{\alpha\alpha} \cdot \vec{v}_{\alpha} = \vec{I}_{\alpha} + \tilde{\vec{i}}_{\alpha}$  with block diagonal admittance matrix  $\tilde{\mathbf{Y}}_{\alpha\alpha}$  of divided subnetworks
- 8. build relation between voltages and currents of removed network:  $\tilde{\vec{e}}_{\psi} = \mathbf{Z}_{\psi\psi} \cdot \vec{\imath}_{\psi}$
- 9. build fundamental equations of Diakoptics:  $\mathbf{Z}_{\psi\psi}\cdot\vec{\imath}_{\psi}=-\mathbf{C}_{\psi\alpha}^{t}\cdot\vec{v}_{\alpha}$

 $\tilde{\mathbf{Y}}_{\alpha\alpha} \cdot \vec{v}_{\alpha} = \vec{I}_{\alpha} + \mathbf{C}_{\alpha\psi} \cdot \vec{i}_{\psi}$ 10. build solution for unknown nodal voltages  $\vec{v}_{\alpha}$ :  $\vec{v}_{\alpha} = \tilde{\mathbf{Y}}_{\alpha\alpha}^{-1} \cdot \left( \vec{I}_{\alpha} - \mathbf{C}_{\alpha\psi} \cdot \tilde{\mathbf{Z}}_{\psi\psi}^{-1} \cdot \mathbf{C}_{\psi\alpha}^{t} \cdot \tilde{\mathbf{Y}}_{\alpha\alpha}^{-1} \cdot \vec{I}_{\alpha} \right)$ with  $\tilde{\mathbf{Z}}_{\psi\psi} = \mathbf{Z}_{\psi\psi} + \mathbf{C}_{\psi\alpha}^t \cdot \tilde{\mathbf{Y}}_{\alpha\alpha}^{-1} \cdot \mathbf{C}_{\alpha\psi}$ 

#### $\mathbf{5}$ Latency Insertion Method (LIM)

- latency generates update equations for branch currents and node voltages
- optimally efficient algorithm, computational effort linear to size of system
- no matrix inversion needed, component by component solved independently
- could be parallelized, which increases simulation speed
- maximum time step  $\Delta t_{max} < \min\left(\sqrt{L_{ij} \cdot C_i}\right)$
- useable as connection tool: many blocks solved with other methods, LIM used for connecting them
  order of calculation: [I<sup>0</sup> → V<sup>1/2</sup> →]I<sup>1</sup> → V<sup>3/2</sup> → I<sup>2</sup> → ...

#### requirements for topology:

- each branch must contain an inductance, otherwise a small inductance is inserted
- each node must provide a capacitive path to ground, otherwise a small shunt capacitance is added

#### leap-frog algorithm:



#### branch algorithm:



$$V_{ij} = V_i - V_j = L_{ij} \cdot \frac{dI_{ij}}{dt} + R_{ij} \cdot I_{ij} - E_{ij}$$
  
$$\iff V_i^{n+\frac{1}{2}} - V_j^{n+\frac{1}{2}} = L_{ij} \cdot \left(\frac{I_{ij}^{n+1} - I_{ij}^n}{\Delta t}\right) + R_{ij} \cdot I_{ij}^n - E_{ij}^{n+\frac{1}{2}}$$
  
$$\iff I_{ij}^{n+1} = I_{ij}^n + \frac{\Delta t}{L_{ij}} \cdot \left(V_i^{n+\frac{1}{2}} - V_j^{n+\frac{1}{2}} - R_{ij} \cdot I_{ij}^n + E_{ij}^{n+\frac{1}{2}}\right)$$

node algorithm:



$$\sum_{k} I_{ik} + G_i \cdot V_i + C_i \cdot \frac{dV_i}{dt} = H_i$$

$$\iff \sum_{k} I_{ik}^n + G_i \cdot V_i^{n+\frac{1}{2}} + C_i \cdot \left(\frac{V_i^{n+\frac{1}{2}} - V_i^{n-\frac{1}{2}}}{\Delta t}\right) = H_i^n$$

$$\iff V_i^{n+\frac{1}{2}} = \frac{\frac{C_i \cdot V_i^{n-\frac{1}{2}}}{\Delta t} + H_i^n - \sum_{k} I_{ik}^n}{\frac{C_i}{\Delta t} + G_i}$$

#### mutual inductance:

- leads to matrix connecting old and new values of both currents
- matrix has to be inverted only once

#### non-linear component:

- handle non-linear behaviour i = f(v) of circuit elements by using iterative Newton-Raphson algorithm
- in branch:  $V^{n+\frac{1}{2}} = f^{-1}(I_{ij}^{n+1})$
- at node:  $I^n = f(V_i^{n+\frac{1}{2}})$
- iterations only on non-linear branches or nodes needed, non-linearity solved locally
- huge computational advantage compared to MNA for non-linear circuit components

#### other circuit elements:

- represented by resistive companion model
- e.g. branch capacitance or shunt inductance (Euler Backward)

# 6 Real-time simulation

- difficult to test a power system device under real conditions or in its working environment
- replace some simulation models of a system by one or several physical components
- controller HIL: low power levels with  $\pm 10$  V
- $\bullet\,$  power HIL: absorbs/sinks real power

### Soft Real-time:

average response time of system is met

### Hard Real-time:

requires that guaranteed response time is met

### Firing Signal Averaging (FSA) method:

- $\bullet\,$  averages external very high frequency signal to simulation time step
- else it can't be tracked by the simulator
- e.g. switching signal of power electronics converter

### conservation of energy at system's boundaries:

- for Power Hardware In the Loop (PHIL)
- power electronics interface between HUT (Hardware Under Test) and ROS (Rest Of System)
- ROS as a model in the simulator
- stability problems/erroneous results may occur due to delays in communication between interface and simulator
- power electronics interface must be much fast than HUT to be transparent, otherwise interferences possible

### algorithm for conservation of energy at system's boundary:

- power electronics hardware interface based on time-variant first order approximation (TFA) of dynamics of HUT
- $\bullet\,$  this compensates for delays introduced by D/A- and A/D-conversion as well as computation