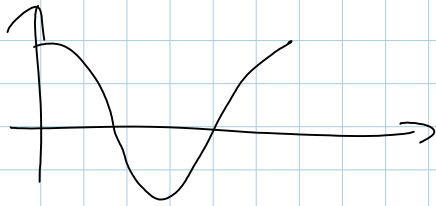


Zusammenfassung:




$$E = E_0 \cos(\omega t + \varphi)$$

$$= \operatorname{Re} \left\{ E_0 \underbrace{e^{j\omega t}}_{\text{zeitl. Platon}} e^{j\varphi} \right\}$$

$$E = E_0 \underbrace{e^{-j\beta z}}_{\text{örtl. Platon}}$$


$$\vec{E} = \vec{E}(x, y, z, t) = \vec{E}(x, y) e^{(y z + j\omega t + \varphi)}$$

$$\gamma = \alpha + j\beta$$


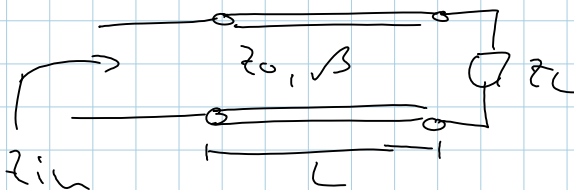


$$Z_{in} = \frac{Z_L + j Z_0 \tan \Theta}{Z_0 + j Z_L \tan \Theta}$$


$$\Theta = \beta L$$

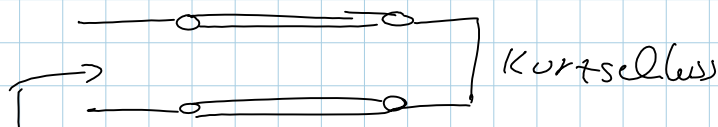

$$Z_{in} = j Z_0 \tan \Theta$$

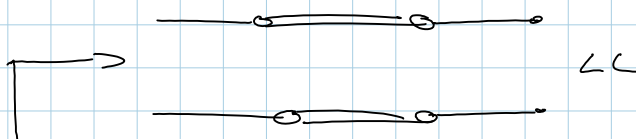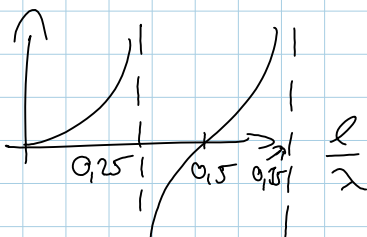

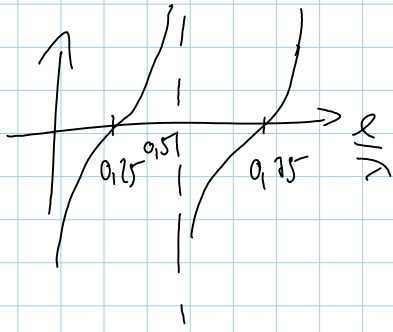
$$Z_{in} \quad Z_{in} = -j Z_0 \cot \Theta$$



Aufgabe 4 H06

4.1.1

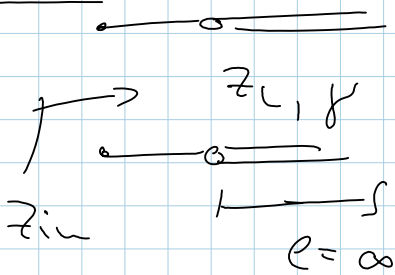


$$Z_{in} = Z_L$$

4.1.2

Ein $\frac{\lambda}{4}$ -Transformator
eine Impedanz Z_A
gemäß der Vorschrift

$$Z_E = \frac{Z_L^2}{Z_A}$$

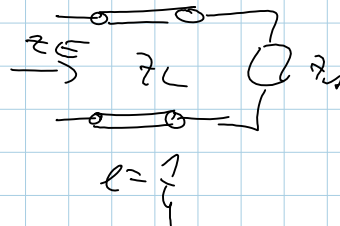

4.1.3

$$P_{\text{verf}} = \frac{|U_g|^2}{8 \operatorname{Re}\{Z_i\}}$$





$$P_L = \frac{1}{2} R_L I^2 = \frac{1}{2} R_L \frac{|U_g|^2}{(R_i + R_L)^2}$$

$$R_i = R_L \Rightarrow P_L = \frac{1}{2} R_L \frac{|U_g|^2}{(2R_L)^2}$$

4.1.4



$$P = \frac{1}{2} \frac{|U|^2}{\operatorname{Re}\{Z\}}$$

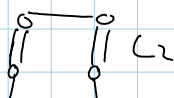

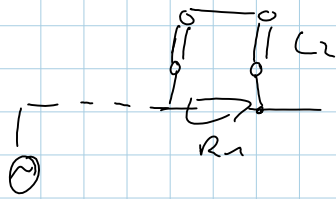

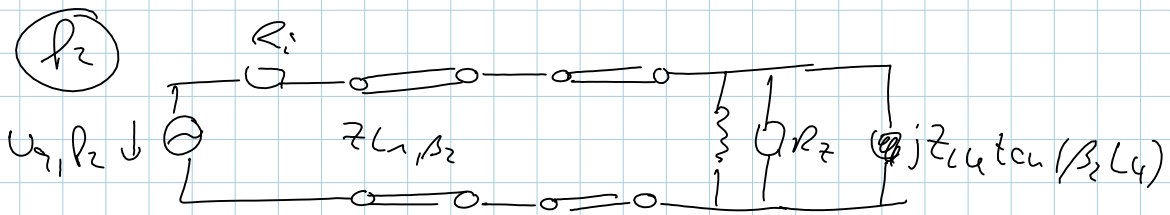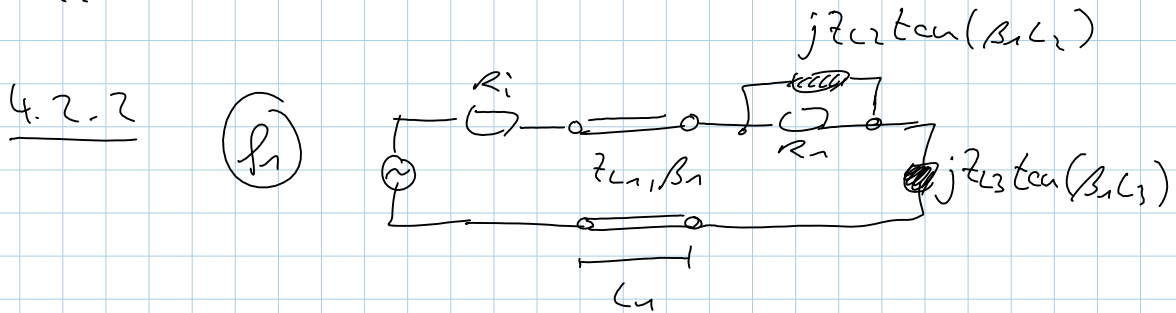4.2.1 $\frac{L_2}{\lambda} = \frac{1}{2} \Rightarrow L_2 = \frac{1}{2} \frac{c_0}{f_2} = 62,5 \text{ nm}$

$\frac{L_4}{\lambda} = \frac{1}{2} \Rightarrow L_4 = \frac{1}{2} \frac{c_0}{f_1} = 50 \text{ nm}$




4.2.3

① Wähle $R_{\text{ref}} = 25 \Omega$

② Start $\frac{R_1}{R_{\text{ref}}} = 4$

Black Magic Design

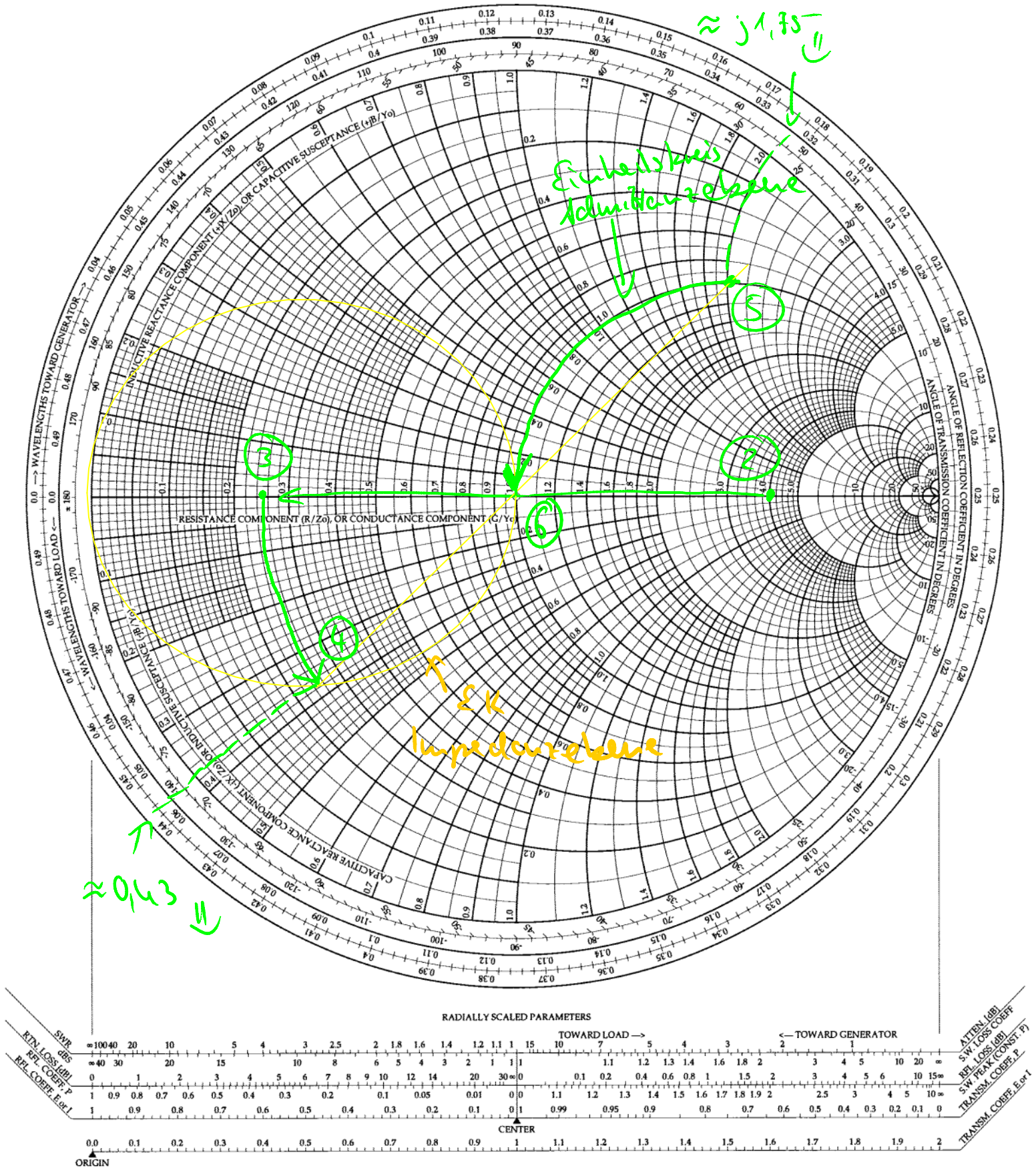

$$\textcircled{3} \quad z \mapsto y \Rightarrow 0,25$$

$$\textcircled{4} \text{ Addition von } -\frac{1}{z_{L2}} \cot(\beta_1 L_2) \cdot R_{\text{ref}}$$

sodass der invertierte Zielkreis
geschnitten wird

$$\textcircled{5} \quad y \mapsto z$$

$$\textcircled{6} \text{ Addition von } j \frac{z_{L3}}{R_{\text{ref}}} \tan(\beta_1 L_3) \text{ sodass}$$

Ziel im Zentrum erreicht wird

Berechnung von z_{L2} und z_{L3} :

$$\text{a) } -\frac{R_{\text{ref}}}{z_{L2}} \cot(\beta_1 L_2) = -j0,43$$

$$\cot\left(\frac{2\pi}{\lambda_1} \frac{\lambda_2}{2}\right) = \cot\left(\pi \frac{f_1}{f_2}\right) = 1$$

$$z_{L2} = \frac{R_{\text{ref}}}{0,43} = 58,14 \, \Omega$$

$$\text{b) } j \frac{z_{L3}}{R_{\text{ref}}} \tan(\beta_1 L_3) = -j1,75$$

$$\tan\left(\frac{2\pi}{\lambda_1} 1,5 \lambda_2\right) = \tan\left(3\pi \frac{f_1}{f_2}\right) = -1$$

$$\Rightarrow z_{L3} = 1,75 \cdot R_{\text{ref}} \\ = \underline{\underline{43,75 \, \Omega}}$$

4.2.4)

$$L_3 = 1,5 \lambda_2$$

$$\begin{aligned}
 j\omega_2 L &= -j Z_{L4} \tan(\beta_2 L_4) \\
 &= -j Z_{L4} \tan\left(\frac{2\pi}{\lambda_2} \underbrace{\frac{L_4}{\lambda_1} \cdot \lambda_1}_{\text{von 4.2.1}}\right) \\
 &= -j Z_{L4} \tan\left(2\pi \frac{L_4}{\lambda_1} \frac{f_2}{f_1}\right) \\
 &= -j 50 \tan\left(2\pi \cdot \frac{1}{2} \cdot 0,8\right) = j 36,32 \Omega
 \end{aligned}$$

$$L = \frac{36,32 \Omega}{\omega_2} = 2,16 \mu\text{H}$$

4.2.5)

$$f_2: \underbrace{Z_E = R_i}_{\text{von 4.2.4.}} \cdot \frac{L_1}{\lambda_2} = 1 \text{ ist Bedingung bereits erfüllt}$$

$$f_1: Z_E = \underbrace{\frac{R_i}{4}}_{\text{von 4.2.3}} \cdot \frac{L_1}{\lambda_1} = \frac{L_1}{\lambda_2} \cdot \frac{\lambda_2}{\lambda_1} = 1,25 \quad \downarrow$$

L_1 ist $\frac{2}{4}$ -Transformator

$$Z_{L1} = \sqrt{Z_E \cdot R_i} = \frac{R_i}{2} = 50 \Omega$$

4.2.6

$$f_1) |U_L|_{f_1} = 0 \quad |I_L|_{f_1} = 0$$

$$\begin{aligned}
 f_2) |U_L|_{f_2} &= \sqrt{P_{\text{Verf.}} \cdot 2 R_2} = \sqrt{\frac{|U_G|^2}{8 R_i} \cdot 2 R_2} \\
 &= \sqrt{\frac{|U_G|^2}{4} \cdot \frac{R_2}{R_i}} = 5 \text{ V}
 \end{aligned}$$

$$|I_L|_{f_2} = \frac{|U_L|_{f_2}}{\omega_2 L} = \frac{5}{36,19} = 138 \mu\text{A}$$

4.2.7

$$f_2) U_E(f_2) = \frac{U_G}{2} = 5 \text{ V}$$

$$\underline{u_1 = 10V} \quad a_2) \quad u_E(1) = \frac{1}{2} = 5V$$

$$\text{weil } \begin{cases} z_E = R_i \\ \frac{L_1}{L_2} = 1 \end{cases}$$

$$b_1) \quad u' = 10V \cdot \frac{R_i}{2R_i} = \frac{10}{2} \quad u = 5V$$

$$u_E(p_1) = u' \sqrt{\frac{R_i}{R_i}} = 2,5V$$