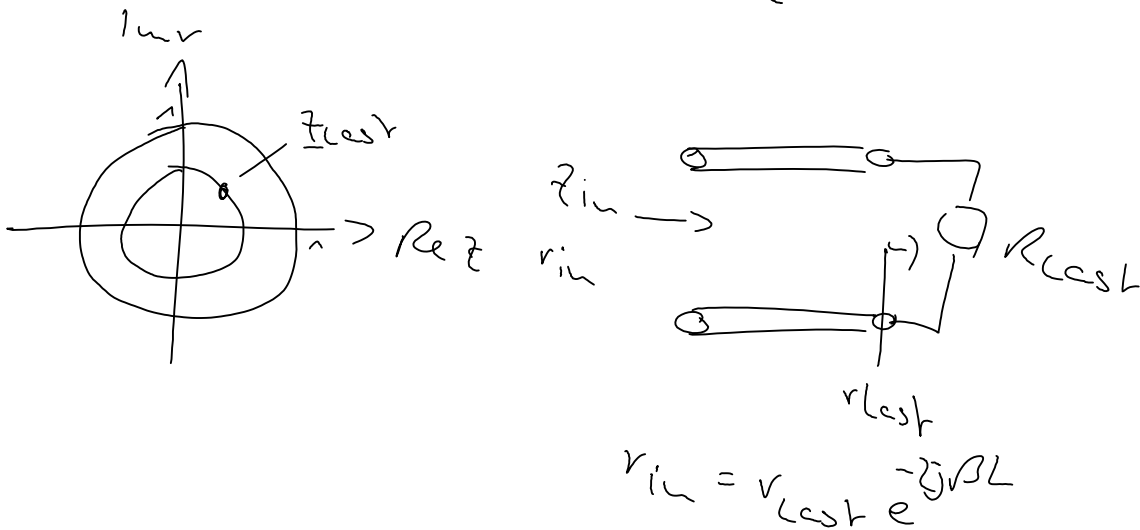
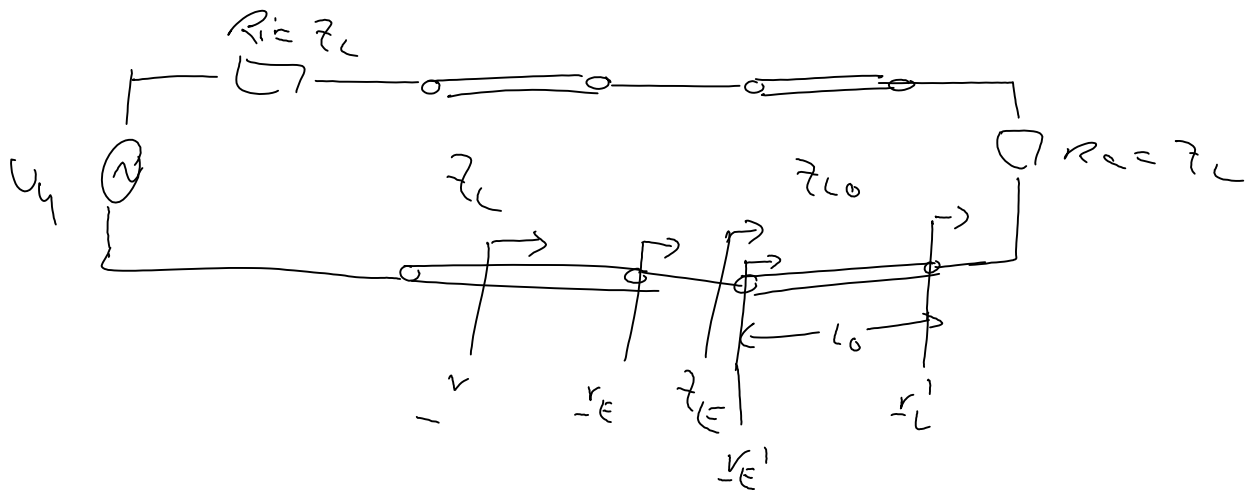


1.5

$$\frac{\lambda}{2} \text{ Trefo}$$

$$Z_{in} = Z_{last}$$

$$r_{in} = r_{last}$$

$$L = n \cdot \frac{\lambda}{2}$$

$$\frac{\lambda}{4} - \text{Trefo} : Z_{in} = \frac{Z_0^2}{Z_{last}}$$

$$Z_{in} = \frac{1}{Z_{last}}$$

$$r_{in} = -r_{last}$$

$$L = n \cdot \frac{\lambda}{2} + \frac{\lambda}{4}$$

2 Minima von $|r|$: $r=0 \Rightarrow r_E=0$

$\Rightarrow z_E = z_L \Rightarrow$ Leitung L_0 ist ein $\frac{\lambda}{2}$ -Trefo

$$L_{0,1} = \frac{u}{2f_1}$$

$$\lambda = \frac{c}{f}$$

$$L_{0,2} = \frac{u}{2f_2}$$

$$u_1 \frac{1}{f_1} = u_2 \frac{1}{f_2}$$

$$\frac{u_1}{u_2} = \frac{f_1}{f_2} = \frac{2}{3}$$

$$L_{0,1} = L_{0,2} = 3 \text{ m}$$

$$f_1 = 100 \text{ MHz}$$

$$f_2 = 150 \text{ MHz}$$

$$\lambda_1 = \frac{c}{f_1} = 3 \text{ m}$$

$$\lambda_2 = 2 \text{ m}$$

$$L_0 = n \cdot \frac{\lambda_1}{2} = (n+1) \frac{\lambda_2}{2}$$

$$\Rightarrow 1,5n = n+1 \Rightarrow n = 2 \quad \Rightarrow \lambda_0 = 3 \text{ m}$$

Maximum von $|r|$ bei $f = 125 \text{ MHz}$

$$\lambda = 2,5 \text{ m}$$

$$\Rightarrow L_0 = 2 \cdot \frac{\lambda}{4} + \frac{\lambda}{4} \Rightarrow \text{Leitung } L_0 \text{ ist ein } \frac{\lambda}{4} \text{ Trafo}$$

$$Z_E = \frac{Z_0^2}{Z_L} = \frac{Z_0^2}{100 \Omega}$$

$$|r| = |r_E| = 0,8$$

$$2 \text{ Fälle: } Z_{L0} > Z_L \text{ und } Z_{L0} < Z_L$$

$$Z_{in} = \frac{Z_0^2}{Z_L} \quad |r_E| = \left| \frac{Z_E - Z_L}{Z_E + Z_L} \right|$$

$$= \left| \frac{Z_{L0}^2 - Z_L^2}{Z_{L0}^2 + Z_L^2} \right|$$

$$Z_{L0} > Z_L: \quad 0,8 = \frac{Z_{L0}^2 - Z_L^2}{Z_{L0}^2 + Z_L^2}$$

$$\Leftrightarrow 0,8 Z_{L0}^2 + 0,8 Z_L^2 = Z_{L0}^2 - Z_L^2$$

$$Z_{L0} = \sqrt{\frac{+1,8 Z_L^2}{+0,2}} = 300 \Omega$$


$$Z_{L0} < Z_L: \quad 0,8 = \frac{-Z_{L0}^2 + Z_L^2}{Z_{L0}^2 + Z_L^2}$$

$$z_{L0}^2 + z_L^2$$

$$0,8 z_{L0}^2 + 0,2 z_L^2 = -z_{L0}^2 + z_L^2$$

$$z_{L0} = \sqrt{\frac{0,2 z_L^2}{1,8}} = 33,3 \Omega$$

A2

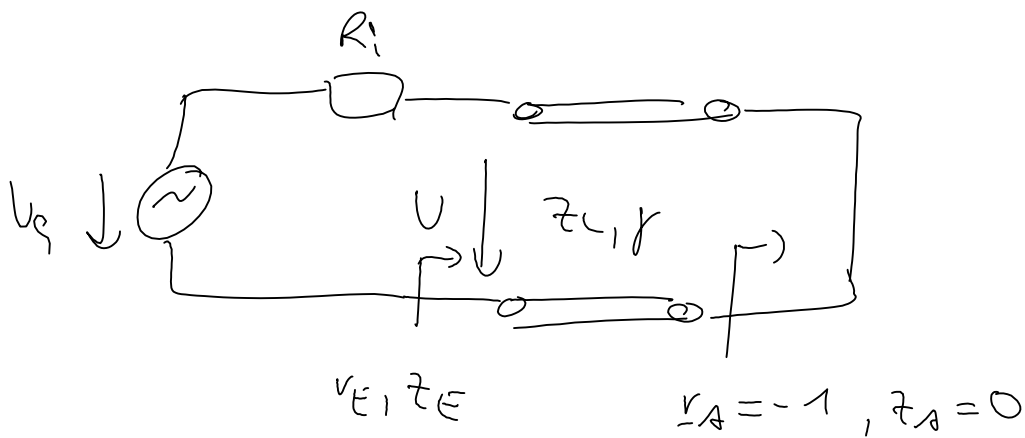

$$\underline{U} = \underline{U}_p + \underline{U}_r \quad (\text{S. 22/23 Script})$$

$$\Rightarrow \frac{\underline{U}}{\underline{U}_p} = 1 + r_E \quad \text{mit} \quad r_E = \frac{\underline{U}_r}{\underline{U}_p}$$

$|\underline{U}|$ max.

für

$$r_E = 1 \quad (\text{Leerlauf})$$

$|\underline{U}|$ minimal

$$r_E = -1 \quad (\text{Kurzschluss})$$

Minimale bei $f = 200 \text{ MHz}$, 200 MHz
 $3 \mu\text{s}$ $1.5 \mu\text{s}$
 durch KS $\rightarrow$ KS $\Rightarrow \frac{7}{2}$ Takte

$$L = n \cdot \frac{7}{2} = \frac{n \cdot c}{2}$$

$$L_n = \frac{L_1}{2} \cdot 3m = \frac{L_2}{2} \cdot 1,5m$$

bei $n_2 = n_1 + 1$ (aufeinanderfolgende
Minim)

$$\frac{u_1}{u_2} = \frac{1.5u}{3u} \Rightarrow u_1 = 1$$

$$\Rightarrow L = \lambda_i \frac{2\pi}{\lambda} = 1,5 \mu$$

Maximum bei $f = 150 \text{ MHz}$ ($\lambda = 2 \text{ m}$)

$$\Rightarrow \frac{7}{4} \text{ Trefo } (KS \rightarrow {}_{11}L^{11})$$

$$v_{in} \approx -v_{L_{eq}} \approx 1$$

$$r_E = \underbrace{r_A}_{-1} \underbrace{e^{-j2L\beta}}_{-1} e^{+2L\alpha} = e^{2L\alpha} \Rightarrow v_E, z_{E, \text{reell}}$$

$$\left| \frac{U}{U_L} \right| = \frac{z_E}{R_i + z_E} \Rightarrow z_E = 0,8 \cdot (R_i + z_E)$$

$$z_E = \frac{0,8 R_i}{0,2} = 41,2 \, \Omega$$

$$r_E = \frac{39}{81} = 0,4753$$

$$\Rightarrow \alpha_{NP} = -\frac{1}{2L} \cdot \ln\left(\frac{39}{81}\right) = \frac{1}{20} \frac{NP}{m}$$

$$\alpha_{dB} = \alpha_{NP} \cdot \frac{20 \text{ dB}}{\underbrace{\ln 10 \cdot NP}_{NP = 8,686 \text{ dB}}} = 3,2387 \frac{\text{dB}}{\text{mm}}$$