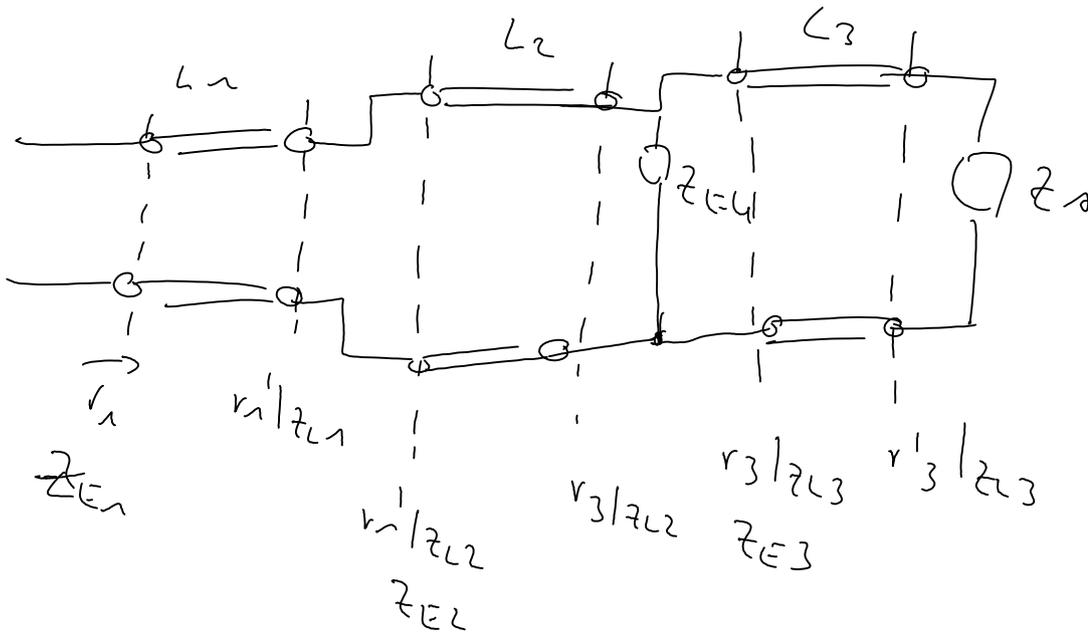


KGÜ 6


Montag, 23. Mai 2011
08:35

AG



The Complete Smith Chart

Black Magic Design

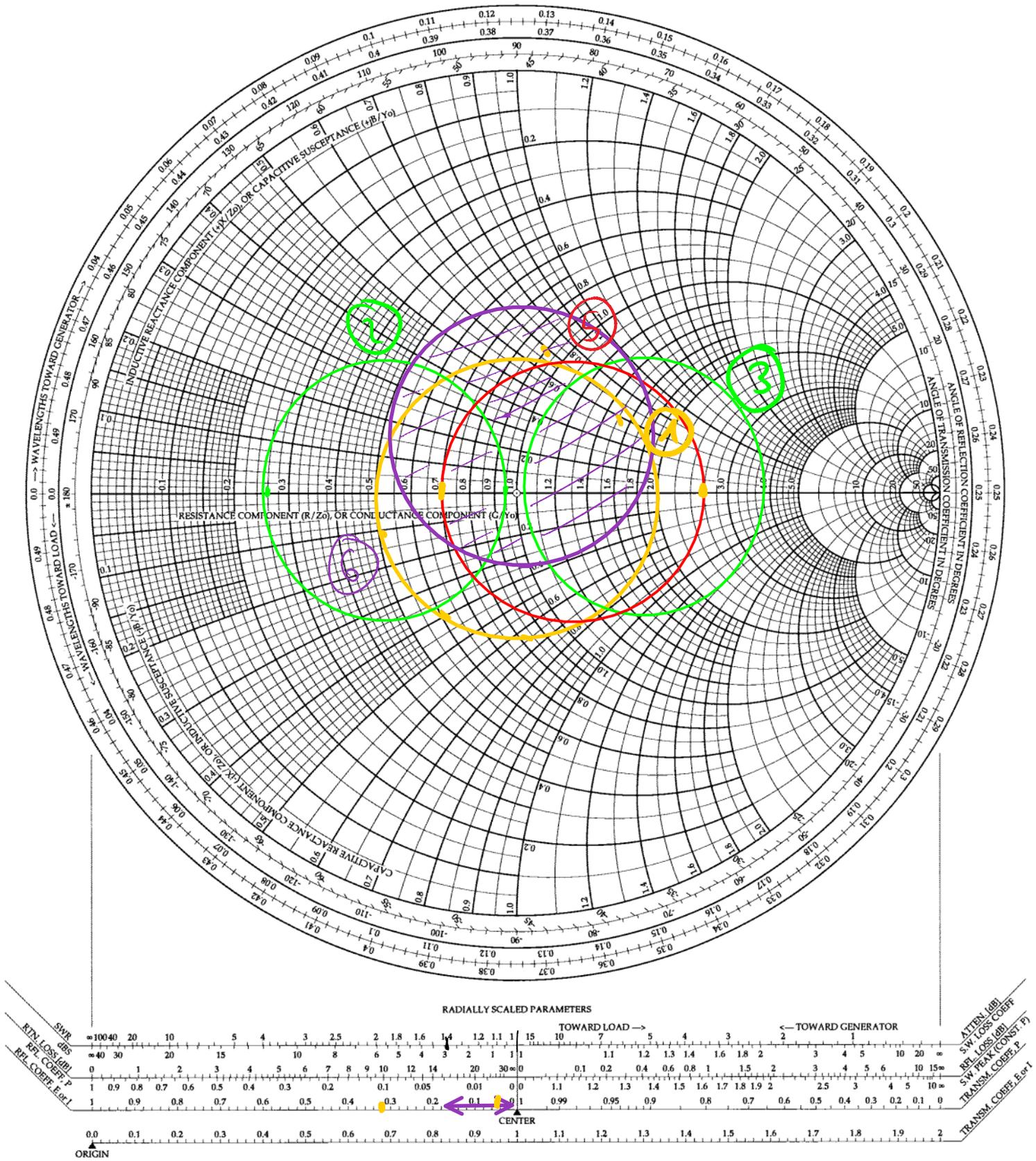

Transformieren über $L1: r_1 \rightarrow r_1'$

$$|r_1'| \leq \frac{1}{6} \quad \text{schreiben}$$

$$|r_1'|_{z_{L1}} = |r_1| \left| e^{2\alpha_{L1} L_1} \right|$$

$$r_1 = r_1' / z_{L1} \cdot e^{-2\gamma L_1}$$

$$|r_1'| = |r_1| \cdot \left| e^{\frac{2 \cdot 15 \text{ dB} / 10 \text{ m}}{8,686 \text{ dB} / 10 \text{ p}} \cdot 18 \text{ m}} \right|$$

$$= 1,8621 \cdot |r_1|$$

$$\frac{L_1}{\lambda_0} = 60$$

$$L_1 = 60 \cdot \frac{c}{f_0} = 18 \text{ m}$$

$$10 \text{ p} = 8,686 \text{ dB}$$

$$|r_1| \leq \frac{1}{6}$$

$$|r_1'| = |r_1| \cdot 1,8621 \leq \left| \frac{1}{6} \right| \cdot 1,8621 \leq 0,3103 \quad \textcircled{1}$$

Kreis $z_{L1} \rightarrow z_{L2}$ umnormieren

$$r_1' / z_{L1} \rightarrow r_1' / z_{L2}$$

$$\omega \frac{L_1}{z_{L1}} \rightarrow \omega \frac{L_2}{z_{L2}} = \frac{z_{L1}}{z_{L2}} = \frac{1}{2} \omega \frac{L_1}{z_{L1}} \quad (z_{L2} = 2 z_{L1})$$

$$\omega \frac{L_1}{z_{L1}} = 1,9 \rightarrow \omega \frac{L_2}{z_{L2}} = 0,95$$

$$\omega \frac{L_1}{z_{L1}} = 0,525 \rightarrow \omega \frac{L_2}{z_{L2}} = 0,2625$$

Kreis $\textcircled{2}$

Transformationen durch L2 ($\frac{\lambda}{4}$ - Trafo)

$$\underline{r_1'} | z_{L2} \rightarrow \underline{r_3} | z_{L2}$$

Kreis (3) = Kreis (4)

Leitung 4

kurzgeschlossen $\Rightarrow r = -1$

$\frac{\lambda}{4}$ - Trafo \Rightarrow Kurzschluss \rightarrow Leerlauf
 \rightarrow ignorieren!

Um normieren $r_3 | z_{L2} \rightarrow r_3 | z_{L3}$

$$\underline{\omega} \frac{L_3}{\varepsilon_3} = \frac{2}{3} \omega \frac{L_2}{\varepsilon_3}$$

$$\omega \frac{L_2}{\varepsilon_2} = 3,9 \quad \Rightarrow \quad \omega \frac{L_2}{\varepsilon_3} = 2,6$$

$$\omega \frac{L_2}{\varepsilon_3} = 1,05 \quad \Rightarrow \quad \omega \frac{L_2}{\varepsilon_3} = 0,7 \quad \text{Kreis (5)}$$

Transformation über L3

$$\frac{L_3}{z_0} = \frac{1}{8} \Rightarrow 90^\circ \text{ Drehung } e^+$$

gegen Uhrzeigersinn

Kreis ⑥

$$|r_3'| z_{L3} = \underbrace{j r_3'}_{e^{j\frac{\pi}{2}}} z_{L3}$$

3.1 $2 \cdot \lambda_n = \lambda_0$

$$\frac{L_n}{\lambda_0} = \frac{L_n}{2\lambda_n} = 60 \Rightarrow \frac{L_n}{\lambda_n} = 120 \quad \frac{\pi}{2} \text{ Treble}$$

$$\frac{L_2}{\lambda_0} = \frac{L_2}{2\lambda_n} = \frac{1}{4} \Rightarrow \frac{L_2}{\lambda_n} = \frac{1}{2} \quad \frac{\pi}{2} \text{ Treble}$$

$$\frac{L_3}{\lambda_0} = \frac{L_3}{2\lambda_n} = \frac{1}{8} \Rightarrow \frac{L_3}{\lambda_n} = \frac{1}{4} \quad \frac{\pi}{4} \text{ Treble}$$

$$\frac{L_4}{\lambda_0} = \frac{L_4}{2\lambda_n} = \frac{3}{4} \Rightarrow \frac{L_4}{\lambda_n} = \frac{3}{2} \quad \frac{\pi}{2} \text{ Treble}$$

$$\alpha_r \sim \sqrt{f} \quad \alpha_s \sim f$$

$$L_4 \quad \frac{\pi}{2} \rightarrow \text{KS} \rightarrow \text{KS}$$

$$L_2 \quad \frac{\pi}{2} \text{ - Verstärkung } \text{KS} \rightarrow \text{KS}$$

$$|r_n(f_n)| = \underbrace{|r_n'| z_{L_n}|}_{\cdot} \cdot \underbrace{e^{-2 \alpha(\lambda_n) L_n}}_{\cdot} = \underline{\underline{0,4757}}$$

$$|r_1(f_1)| = \underbrace{|r_1|}_{|r_1|=1} \cdot \underbrace{|z_{L1}|}_{=0,4151} \cdot \underbrace{|C|}_{=0,4151}$$

$$d_1(f_1) = \sqrt{2} d_1(f_0)$$

1.2) $|r| \approx 0,18$

$$S = USWR = 1,4$$

$$\Rightarrow |r| = \frac{1}{6}$$

$$S = \frac{1+|r|}{1-|r|} \Leftrightarrow S(1-|r|) = 1+|r|$$

$$|r| = \frac{S-1}{S+1} = \frac{1}{6}$$

1.4) $\frac{P_1}{d_1} = 3,49$

1.5) $\epsilon_r' = 5,427$