
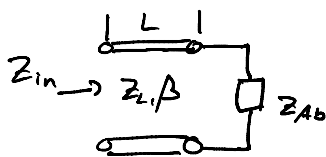


3.3.1 $\frac{L_2}{\lambda_2} = \frac{1}{4}$ (an den klemmen B entsteht ein Kurzschluss für $f=f_2$)

3.3.2. $\frac{L_2}{\lambda_1} = \frac{L_2}{\lambda_2} \cdot \frac{\lambda_2}{\lambda_1} = \frac{L_2}{\lambda_2} \cdot \frac{f_1}{f_2} = \frac{1}{4} \cdot \frac{1}{2} = \frac{1}{8}$

ESB: (f1)

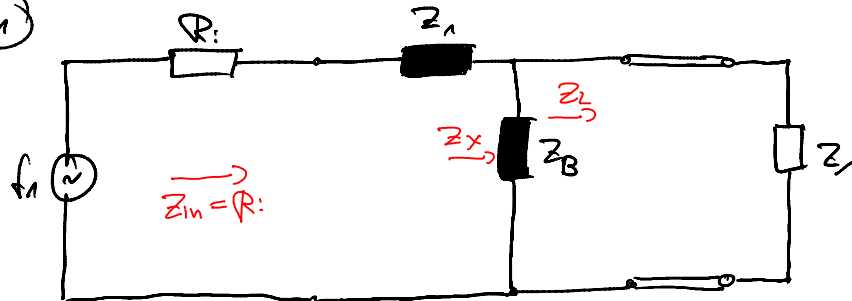

$$Z_{in} = \frac{Z_{AB} + j Z_L \tan(\beta L)}{1 + j \frac{Z_{AB}}{Z_L} \tan(\beta L)}$$


$$Z_B = -j Z_L \cot(\beta L_2)$$

$$Z_B(f_2) = -j Z_L \cot\left(\frac{2\pi}{\lambda_2} L_2\right) = 0$$

$$Z_B(f_1) = -j Z_L \cot\left(\frac{2\pi}{\lambda_1} L_2\right) = -j Z_L$$

$$\Gamma_B(f_2) = -1$$

$$\Gamma_B(f_1) = -j$$

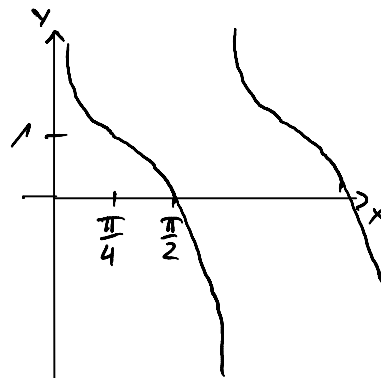

1.) $R_N = Z_L$


2.) R_i einzeichnen (START)
 $\overline{R_N}$

3.) $\frac{Z_A}{R_N}$ einzeichnen

4.) $Z \rightarrow Y$

5.) $Y_B \cdot R_N = +j$ abziehen

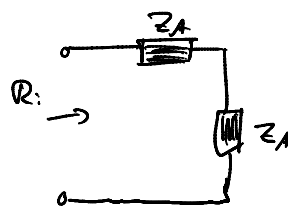
6.) $Y \rightarrow Z \Rightarrow \frac{Z_C}{Z_L}$



$$\frac{Z_x}{R_N} = \frac{R_i}{R_N} - \frac{Z_A}{R_N}$$

$$Z_A = -j Z_L \cot(\beta_1 L_1)$$

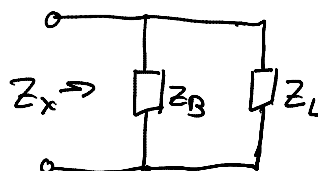
$\underbrace{\quad}_{0 \dots \infty > 0}$



$$Y_C R_N = Y_x R_N - Y_B R_N$$

3.3.4.)

7.)

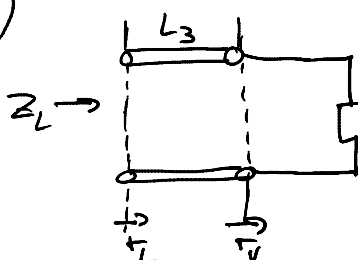

$$\Gamma_V = \Gamma_L e^{+2j\beta_1 L_3}$$