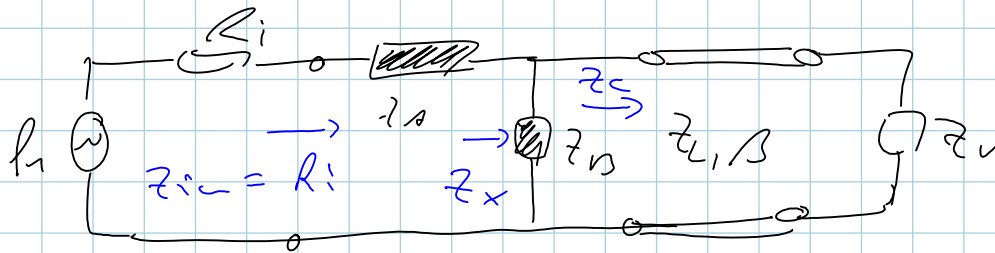


3.3.1 $\frac{L_2}{\lambda_2} = \frac{1}{4}$ (an Klemme B entsteht ein Kurzschluss für $l = l_2$)

3.3.2) $\frac{L_2}{\lambda_1} = \frac{L_2}{\lambda_2} \cdot \frac{\lambda_2}{\lambda_1} = \frac{L_2}{\lambda_2} \cdot \frac{l_1}{l_2}$

$$= \frac{1}{4} \cdot \frac{1}{2} = \frac{1}{8}$$


Es B l_1



$$Z_B = -j Z_L \cot(\beta L_2)$$

$$Z_B(l_2) = -j Z_L \cot\left(\frac{2\pi}{\lambda_2} L_2\right) = 0$$
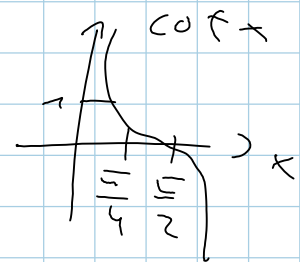
$$Z_B(l_1) = -j Z_L \cot\left(\frac{2\pi}{\lambda_1} L_2\right) = -j Z_L$$



$$r_B(l_2) = -1$$

$$r_B(l_1) = -j$$

3.3.3)

1.) $R_N = Z_L$

2.) $\frac{R_i}{R_N}$ einzeichnen (START)



Eingefügt aus: <file:///D:/Uni/SmithChartNeu.pdf>

Name: _____


Smith-Diagramm (Widerstandsform)

Zu Aufgabe

Nr.: _____


Normierungs-
widerstand

$R_N =$ _____

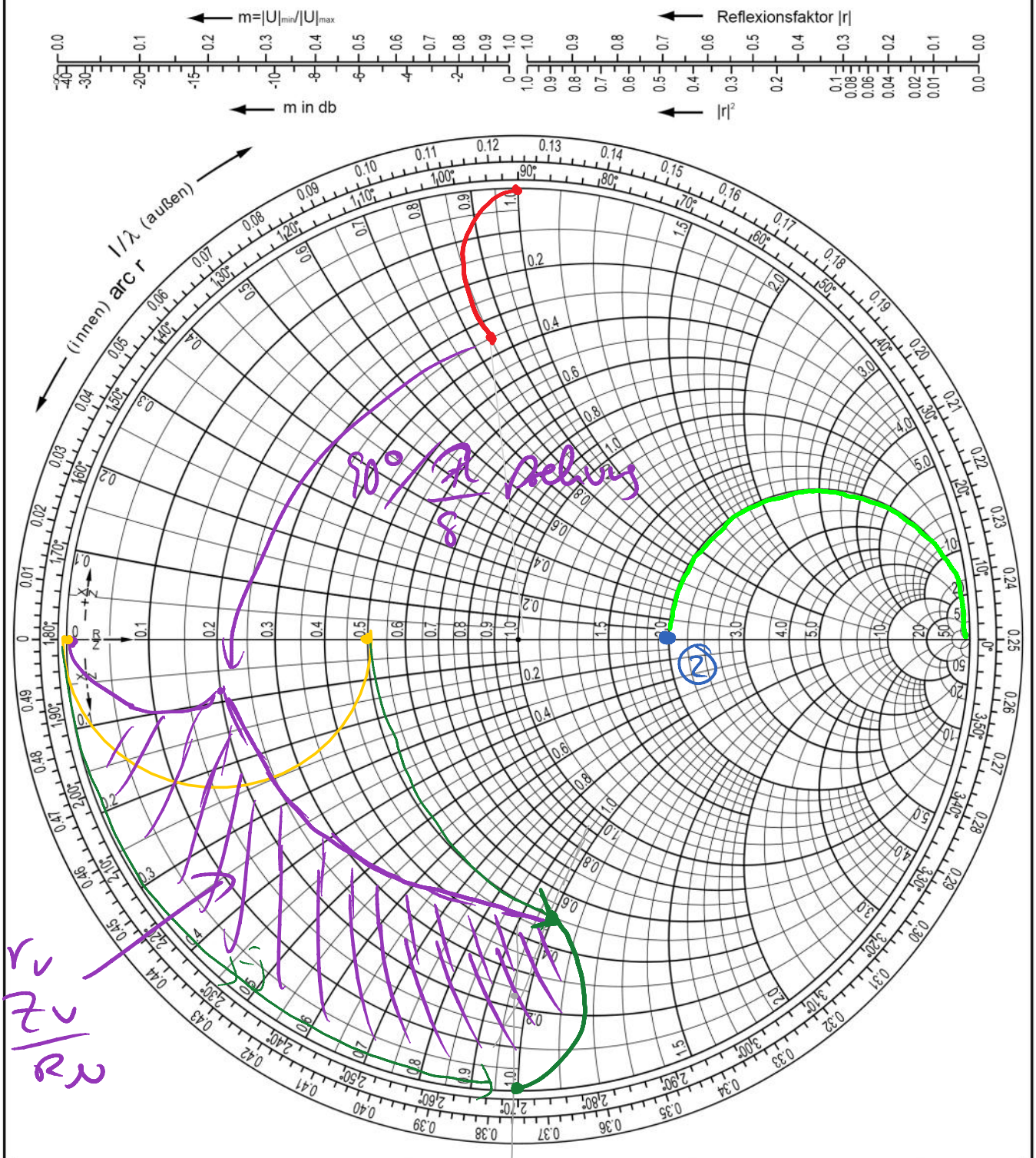


Erläuterungen zum Transformationsweg:

3.) $\frac{z_A}{R_N}$ abziehen

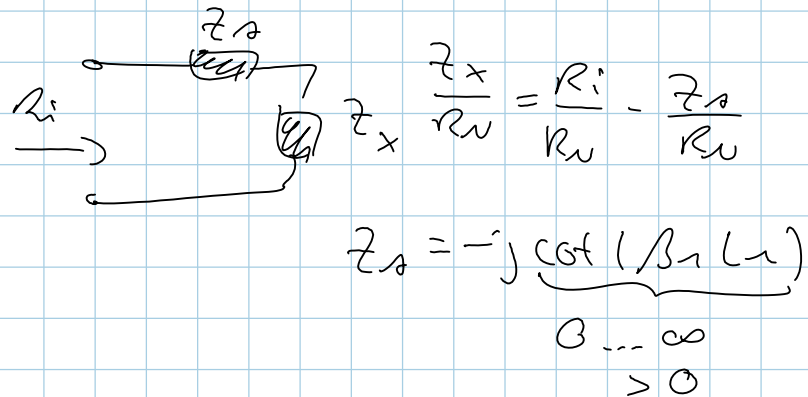


4.) $z \rightarrow y$

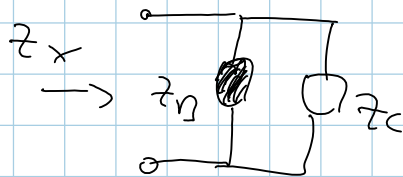

5.) $y_c R_N = y_x R_N - y_B R_N$
 $y_B \cdot R_N = +j$ abziehen

6.) $y \rightarrow z \Rightarrow \frac{z_c}{z_L}$

3.3.4 1.)

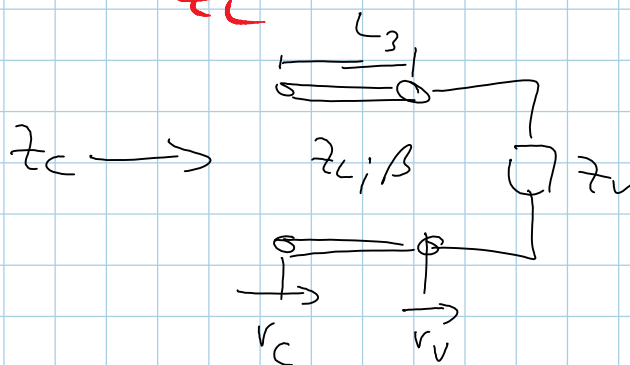

$$r_v = r_c e^{2j\beta_1 L_3}$$