

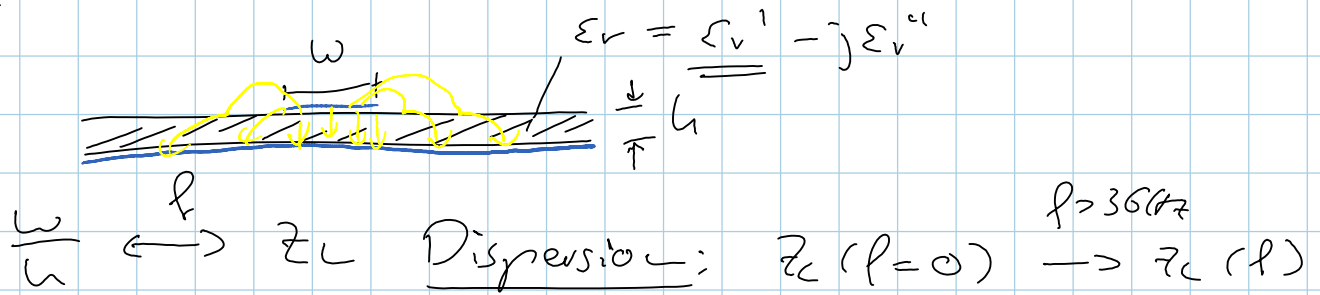


4.1

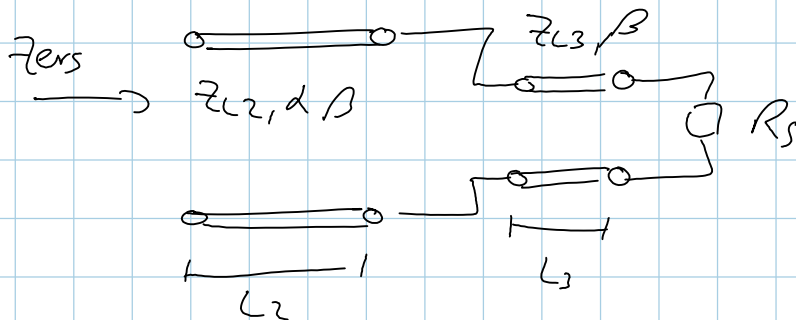



$\epsilon_{\text{refl}}(\epsilon_r; h, \omega; \frac{\omega}{h})$ $\epsilon_{\text{refl}}(f=0) \xrightarrow{f > 36 \text{ kHz}} \epsilon_{\text{refl}}(f)$


4.1.1

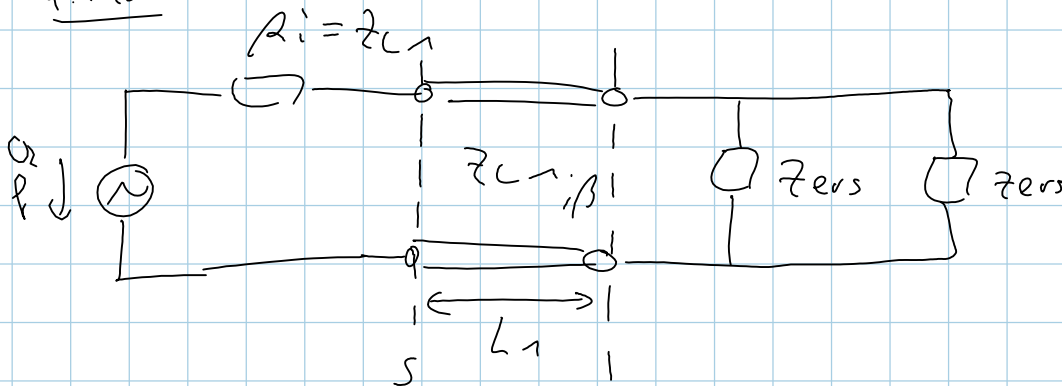

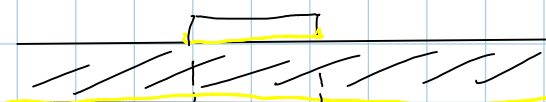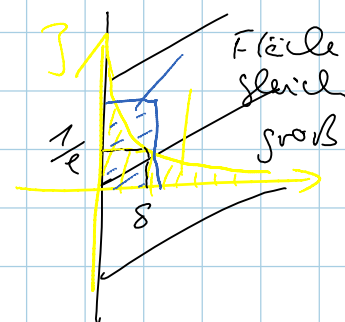4.1.2)

$$\delta = \frac{1}{\sqrt{\epsilon_r \mu_0}} = 0,661 \mu\text{m}$$





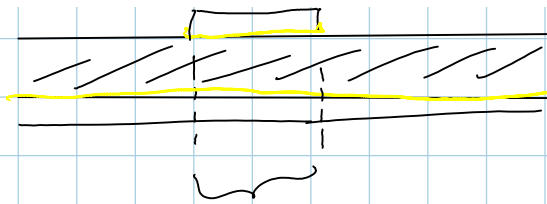

Strom führender Bereich

4.1.3)


$$Z_{L1} = 50 \Omega$$

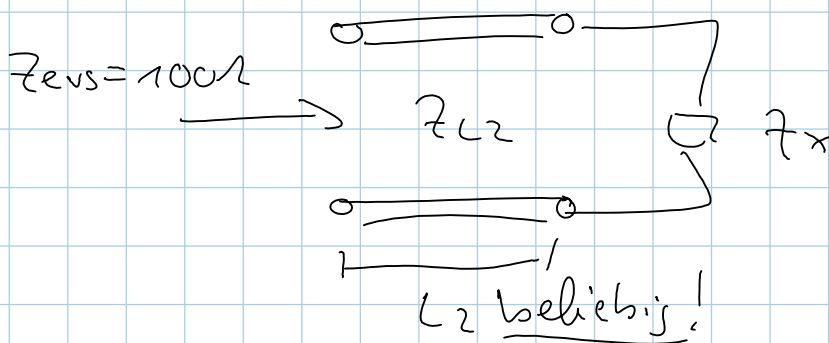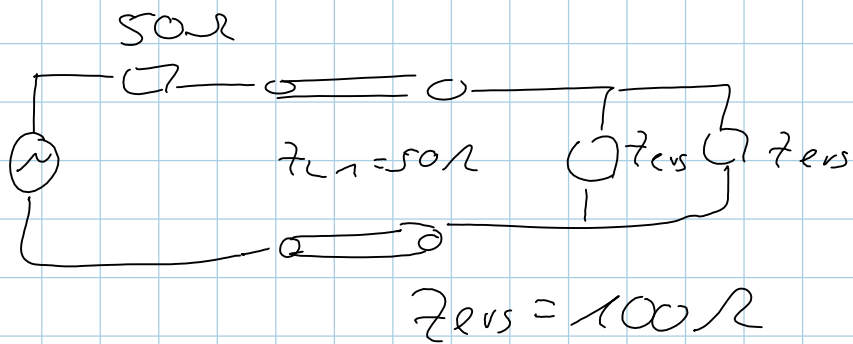

$$Z_{L2} = 100 \Omega$$

$$Z_x = 100 \Omega$$
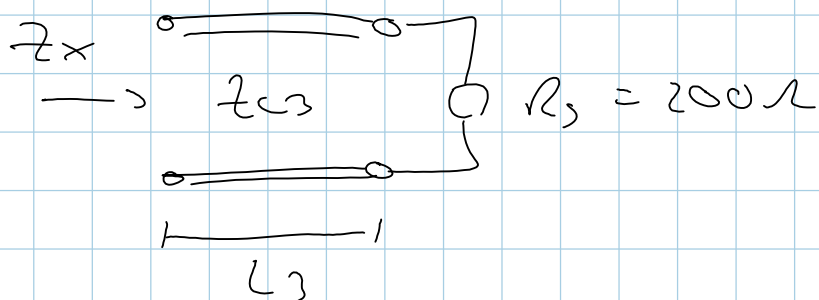
$$r_2 = r_1 \cdot e^{-2j\beta L_2} = 0 \Rightarrow Z_{L2} = Z_x$$



$$Z_{L3} = \sqrt{Z_R \cdot R_3} = 141 \Omega$$

$$\frac{L_3}{Z_{L3}} = \frac{1}{4}$$

$$Z_L = \frac{Z_0}{\sqrt{\epsilon_{\text{rel}}}}$$

$$Z_{L2} = 100 \Omega \quad \frac{\omega}{\omega_0} = 1 \quad (\text{S. 22 Schnitt})$$