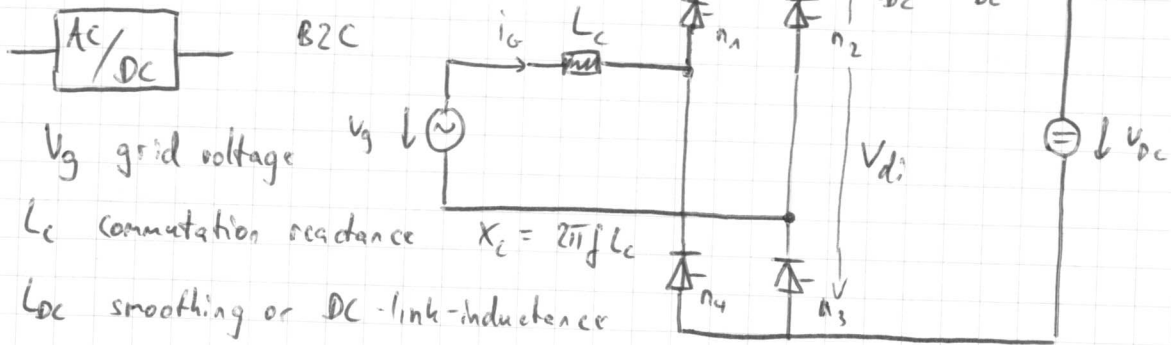


Line Commutated Converters

 V_g grid voltage L_c commutation reactance $X_c = 2\pi f L_c$ L_{dc} smoothing or DC-link-inductance

$$X_{dc} = 2\pi f L_{dc}$$


 V_{dc} = output voltage

general assumptions

- V_g purely sinusoidal, no internal resistance
- V_{dc} is constant, in steady-state $\bar{V}_{di} = V_{dc}$ ($\bar{V}_{L_{dc}} = 0$)
- n_1 & n_3 are fired at $\omega t = \alpha$
- n_2 & n_4 " " " $\omega t = \alpha + \pi$
- all other parasitic effects are neglected
- periodic operation

Thyristor

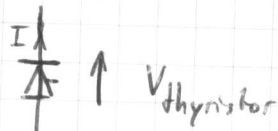- can be fired, if $V_{thyristor} > 0$
- turns off automatically at zero crossing of the current
- $I_{thyristor} > 0$ (always!)



① Idealized Calculations

a) $L_c = 0$ b) $L_{dc} \rightarrow \infty \Rightarrow I_{dc} = \text{const.}$


$$\bar{V}_{di} = \frac{1}{2\pi} \int_0^{2\pi} V_g(\omega t) d(\omega t)$$

$$= \frac{1}{2\pi} \int_0^{2\pi} \sqrt{2} V_g \sin(\omega t) d(\omega t)$$

$$\stackrel{\text{Symmetric}}{=} \frac{1}{\pi} \int_0^{\pi} \sqrt{2} V_g \sin(\omega t) d(\omega t)$$

$$= \left[\frac{\sqrt{2}}{\pi} V_g (-\cos(\omega t)) \right]_0^{\pi}$$
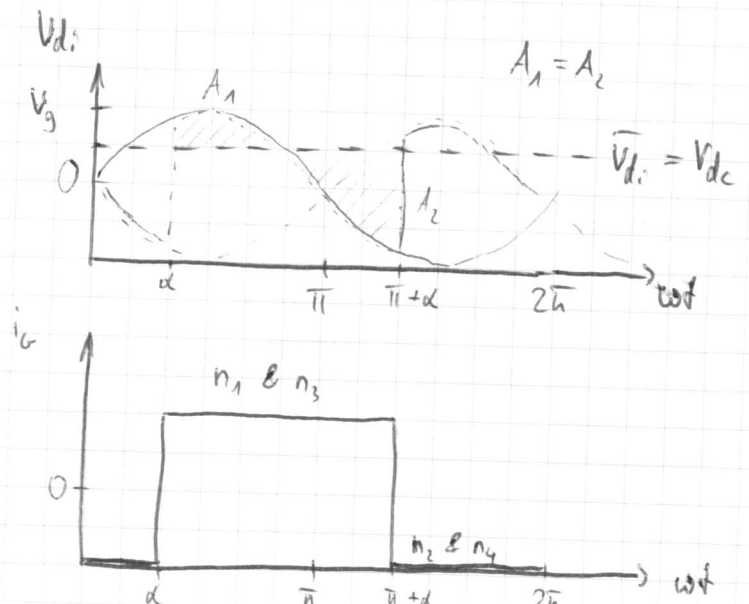
$$= \frac{\sqrt{2}}{\pi} V_g [\cos \alpha - \underbrace{\cos(\alpha + \pi)}_{-\cos \alpha}] = \frac{2\sqrt{2}}{\pi} V_g \cos \alpha$$




$0^\circ < \alpha < 90^\circ \Rightarrow \bar{V}_d > 0, I_{dc} > 0 \Rightarrow \text{Rectifier}$
 $90^\circ < \alpha < 180^\circ \Rightarrow \bar{V}_d < 0, I_{dc} < 0 \Rightarrow \text{Inverter}$

b) $L_c \rightarrow \infty \Rightarrow I_{dc} = \text{const.}$

a) $L_c \neq 0 \Rightarrow$ no instantaneous commutation $\Rightarrow$ all thyristors conduct during commutation
 $\Rightarrow V_c = V_g \Rightarrow$ Input of $B_2 C = 0V$

② Conventional calculations

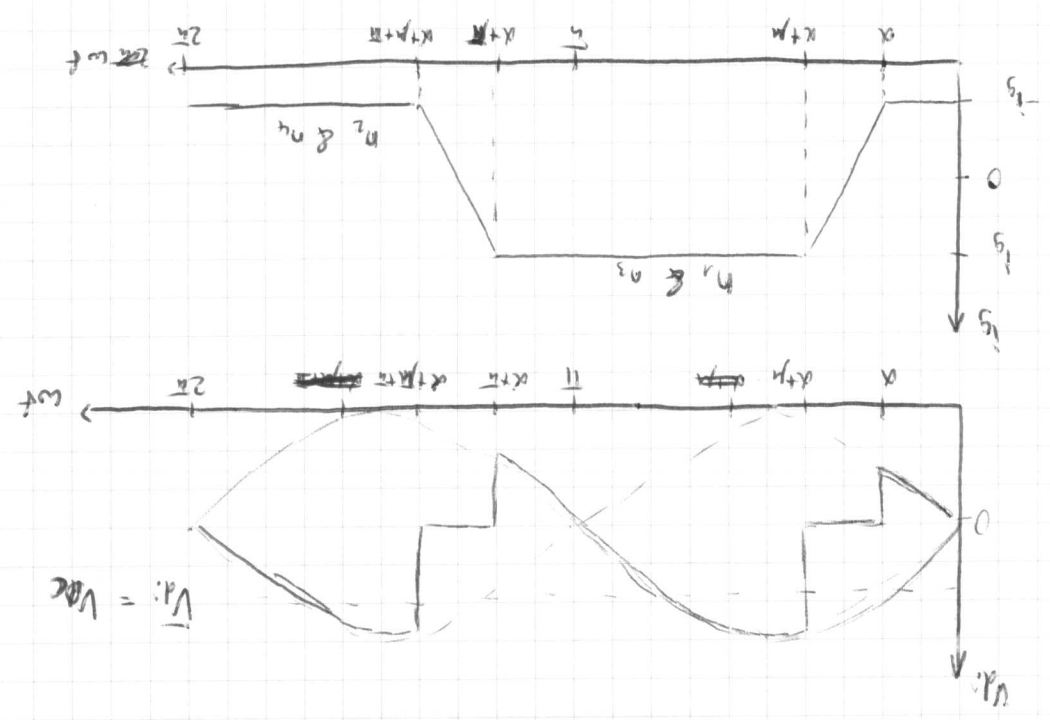

Calculation of the commutation

$$V_c = L_c \frac{di_g(t)}{dt} = \int_{\alpha}^{\alpha+\mu} L_c \frac{di_g(t)}{dt} dt = \int_{\alpha}^{\alpha+\mu} L_c \frac{d}{dt} (I_{dc} \frac{t - \alpha}{\mu}) dt = \frac{L_c I_{dc}}{\mu} \int_{\alpha}^{\alpha+\mu} dt = \frac{L_c I_{dc} \mu}{\mu} = L_c I_{dc}$$

Integration/Substitution

$y = \omega t \Rightarrow y' = \frac{dy}{dt} = \omega \Rightarrow dt = \frac{dy}{\omega}$
 $\omega = \frac{d\omega t}{dt} \Rightarrow dt = \frac{d\omega t}{\omega}$

$\Rightarrow$ new boundaries multiplied by ω

$$i_g(y) = \int_{\alpha+\mu}^{\alpha} \frac{L_c}{\omega} \frac{d}{dy} \left(\frac{I_{dc}}{\mu} y \right) dy = \int_{\alpha+\mu}^{\alpha} \frac{L_c}{\omega} \frac{I_{dc}}{\mu} dy = \frac{L_c I_{dc}}{\omega \mu} \int_{\alpha+\mu}^{\alpha} dy = \frac{L_c I_{dc}}{\omega \mu} (\alpha - \alpha - \mu) = -\frac{L_c I_{dc} \mu}{\omega \mu} = -\frac{L_c I_{dc}}{\omega}$$

$\Rightarrow 2 I_{dc} = \int_{\alpha+\mu}^{\alpha} \frac{L_c}{\omega} \frac{d}{dy} \left(\frac{I_{dc}}{\mu} y \right) dy = \int_{\alpha+\mu}^{\alpha} \frac{L_c}{\omega} \frac{I_{dc}}{\mu} dy = \frac{L_c I_{dc}}{\omega \mu} \int_{\alpha+\mu}^{\alpha} dy = \frac{L_c I_{dc}}{\omega \mu} (\alpha - \alpha - \mu) = -\frac{L_c I_{dc} \mu}{\omega \mu} = -\frac{L_c I_{dc}}{\omega}$

$\rightarrow$ calculation of commutation angle μ
 $\rightarrow$ output voltage

③ Detailed Calculation

a) $L_c \neq 0$ $L_{dc} \rightarrow \infty \Rightarrow$ Exercise IIB6C

general assumptions:

- three phase system is balanced

- V_{dc} is constant $\bar{V}_{dia} = V_{dc}$ - n_1, n_6 are ideal thyristors $\Rightarrow$ always two thyristors are on-state

- firing angles

 $n_1 \quad \alpha \quad n_2 \quad \alpha + 60^\circ$ $n_3 \quad \alpha + 120^\circ \quad n_4 \quad \alpha + 180^\circ$ $n_5 \quad \alpha + 240^\circ \quad n_6 \quad \alpha + 300^\circ$ $1, 2 \rightarrow 2, 3 \rightarrow 3, 4 \rightarrow 4, 5 \rightarrow 5, 6 \rightarrow 6, 1 \rightarrow 1, 2 \dots$

① Idealized Calculations

a) $L_c = 0$ b) $L_{dc} \rightarrow \infty \Rightarrow I_{dc} = \text{const.}$ Period = $60^\circ = \frac{\pi}{3}$ $V_{dia}(t) = V_+ - V_- \hat{=}$ line to line Voltage $V_{ic} = \{V_{12}, V_{23}, V_{31}; -V_{12}, -V_{23}, -V_{31}\}$

$$\bar{V}_{dia} = \frac{1}{\pi/6} \int_{\alpha/\omega}^{(\alpha+60^\circ)/\omega} V_{12}(t) dt = \frac{3\sqrt{2}}{\pi} V_{12} \cdot \cos \alpha$$

$\searrow$ line to line rms

 $\alpha < 90^\circ \Rightarrow$ Rectifier $\alpha > 90^\circ$ Inverter

② Conventional Calculations


a) $L_c \neq 0$ b) $L_{dc} \rightarrow \infty$ $\rightarrow$ compare B2C

$$\bar{V}_{dia} = \frac{3\sqrt{2}}{\pi} V_{LL} (\cos \alpha - \frac{X_{Lc} I_{dc}}{\sqrt{2} V_{LL}})$$

calculation of the current

• commutation from n_1 to n_3 ($\omega t = \alpha + 120^\circ$) n_1 & n_2 are conducting

$$\Rightarrow V_+ = V_1 \quad \Rightarrow V_- = V_2 \quad \Rightarrow V_{di} = V_{12}$$

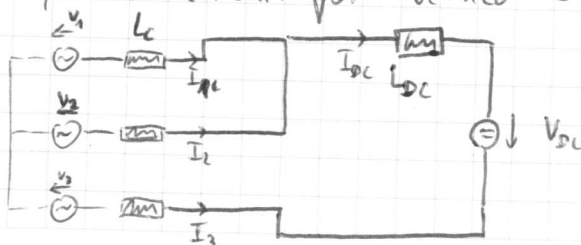 $\omega t = \alpha + 120^\circ \rightarrow n_3$ is fired $\rightarrow$ new equivalent circuit for $\alpha + 120^\circ \leq \omega t \leq \alpha + \mu + 120^\circ$ before commutation: $\omega t = \alpha$


$$I_1 = I_{dc}, \quad I_2 = 0, \quad I_3 = -I_{dc}$$

after commutation: $\cancel{I_x} \omega t = \alpha + \mu$

$$I_1 = 0, I_2 = I_{DC}, I_3 = -I_{DC}$$

→ no voltage drop across L_3 , $\frac{dI}{dt} = 0$

new equivalent circuit

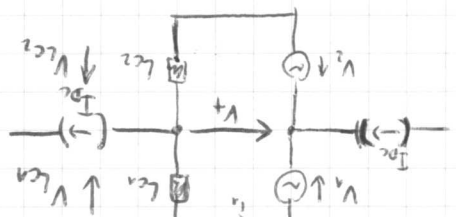

$$I_1 + I_2 = I_{DC} = \text{const}$$

$$V_2(t) = L_2 \cdot \frac{dI_2(t)}{dt}$$

$$I_2(t) = I_{DC} - I_1(t)$$

$$\Rightarrow V_2(t) = 2X_L \frac{dI_1(t)}{dt}$$

$$\Rightarrow I_1(t) = \frac{1}{2X_L} \int_{\omega t}^{\alpha} \sqrt{2} V_{gnd} \sin(\omega t) d(\omega t) = \sqrt{2} V_{gnd} / 2X_L (\cos \alpha - \cos \omega t)$$

I_1 for a half period

$$I_1(\omega t) = \begin{cases} \sqrt{2} V_{gnd} / 2X_L (\cos \alpha - \cos \omega t) & \alpha < \omega t < \alpha + \mu \\ I_{DC} & \alpha + \mu < \omega t < \alpha + \frac{3}{2}\pi \\ I_{DC} - \sqrt{2} V_{gnd} / 2X_L [\cos \omega t - \cos(\omega t - \alpha + \frac{3}{2}\pi)] & \text{otherwise} \end{cases}$$

$$\alpha + \frac{3}{2}\pi < \omega t < \alpha + \frac{3}{2}\pi + \mu$$

Exercise B B.1) Smoothing inductance to reduce the current ripple

$$B.2) \quad \bar{I}_{DC} = 2 \text{ kA} \quad V_{DC} = 260 \text{ kV} \quad R_{DC} = 0 \quad \bar{V}_{L_{DC}} = 0 \quad V_{DC} = \bar{V}_{d,\alpha} = \frac{3 \cdot \sqrt{2}}{\pi} \sqrt{3} \cdot V_{A0} \cdot \left(\cos \alpha - \frac{\omega L_{DC} \cdot \bar{I}_{DC}}{\sqrt{3} \cdot \sqrt{2} \cdot 220 \text{ kV}} \right)$$

$$V_{DC} = \dots = \frac{3 \sqrt{2}}{\pi} \sqrt{3} \cdot 220 \text{ kV} (\cos \alpha) - \frac{2\pi \cdot 50 \text{ Hz} \cdot 1,5 \text{ mH} \cdot 2 \text{ kA}}{\sqrt{3} \cdot \sqrt{2} \cdot 220 \text{ kV}}$$

$$C) \quad \cos \alpha = 0,507 \Rightarrow \alpha = 59,536^\circ$$

$$\cos(\alpha) - \cos(\alpha + \mu) = \frac{2 X_L \cdot \bar{I}_{DC}}{\sqrt{2} \sqrt{3} V_{A0}}$$

$$\Rightarrow \mu = \cos^{-1} \left(\cos \alpha - \frac{2 X_L \bar{I}_{DC}}{\sqrt{2} \sqrt{3} V_{A0}} \right) - \alpha = 0,0232^\circ$$

B.3) see diagram

$$B.4) \quad \alpha \approx 60^\circ \quad 59,536^\circ \quad R_{DC} = 0,01 \Omega$$

$$\text{From DC} \quad P_{AC} = V_{DC,r} \cdot \bar{I}_{DC,r} + \bar{I}_{DC,r}^2 \cdot R_{DC}$$

$$= 260 \text{ kV} \cdot 2 \text{ kA} + (2 \text{ kA})^2 \cdot 0,01 \Omega = 520,04 \text{ MW}$$

$$P_{AC} = 3 \cdot V_{A0} \cdot \bar{I}_A \cdot \cos \alpha$$

$$\bar{I}_A = \frac{V_{DC,r} \cdot \bar{I}_{DC,r} + \bar{I}_{DC,r}^2 \cdot R_{DC}}{3 V_{A0} \cdot \cos \alpha} = 1,554 \text{ kA}$$

$$Q = 3 \cdot V_{A0} \cdot \bar{I}_A \cdot \sin \alpha$$

$$= 884,123 \text{ MVar}$$

$$B.5) \quad S = 3 \cdot V_{A0} \cdot \sqrt{\frac{2}{3}} \cdot \bar{I}_{DC,r} = 1077 \text{ MVA}$$

$$S^2 = P^2 + Q^2 + D^2$$

$$D = \sqrt{S^2 - P^2 - Q^2} = 320,386 \text{ MVA}$$

B.6) see solution

B.7) γ , the hold-off interval

$$B.8) \quad R_{DC} \neq 0 \quad V_{DC,min} = 0 \quad V_{DC,max} = \frac{3 \sqrt{2}}{\pi} \sqrt{3} \sqrt{V_{A0}} \left(1 - \frac{\omega L_{DC} \cdot \bar{I}_{DC}}{\sqrt{3} \sqrt{2} \cdot V_{A0}} \right) - R_{DC} \cdot \bar{I}_{DC}$$

$$= 513,72 \text{ kV}$$

B.9) losses should be minimized ($\bar{I}_{DC}^2 \cdot R_{DC}$)

$$\Rightarrow V_{DC,max}$$

$$P = V_{DC} \cdot \bar{I}_{DC} = 500 \text{ MW} \Rightarrow \bar{I}_{DC} = 972,33 \text{ A}$$

$$\Rightarrow P_v = \bar{I}_{DC}^2 \cdot R_{DC} = (972,33 \text{ A})^2 \cdot 0,01 \Omega = 9,473 \text{ kW}$$

B.10)

Physist Ex. 8

$S_{ac} = \sqrt{3} \cdot U_{LL} \cdot I_{rms}$ (not I , $\sqrt{3} I$)
 Current as in Fig. 5.18 (LV) Rectangular waveform
 $I_{rms} = \sqrt{\frac{1}{2\pi} \int_0^{2\pi} i^2(\omega t) d\omega t} = \sqrt{\frac{1}{2\pi} \int_0^{2\pi} I_{dc}^2 d\omega t} = \sqrt{\frac{1}{2\pi} \cdot 2\pi \cdot I_{dc}^2} = I_{dc}$


Day 2 DC-DC Converter

A) Buck Converter


B) Boost Converter

Steady state analysis is based on a periodic operation with a period $T_s = \frac{1}{f_s}$
 All system quantities have to be same at $t=0$ and $t=T_s$
 $\Rightarrow 0 = \int_0^{T_s} V_L(t) dt = \int_0^{T_s} L \frac{di_L}{dt} dt$


i.e. real loads

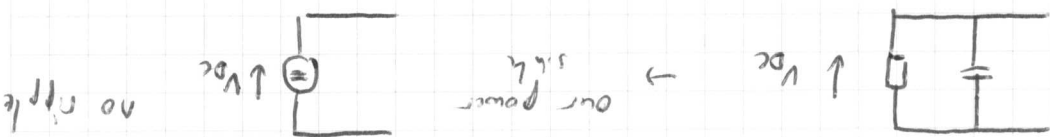

our power

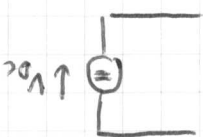

no ripple


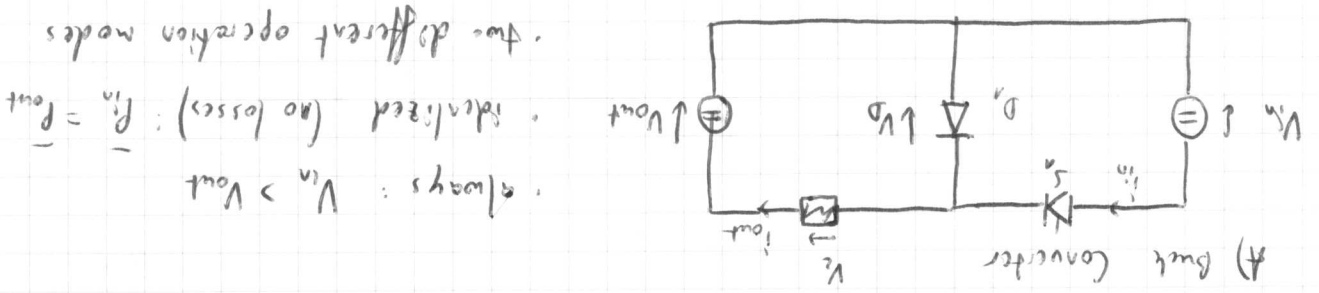


A) Buck Converter

two different operation modes
 idealized (no losses): $P_{in} = P_{out}$
 always: $V_{in} > V_{out}$

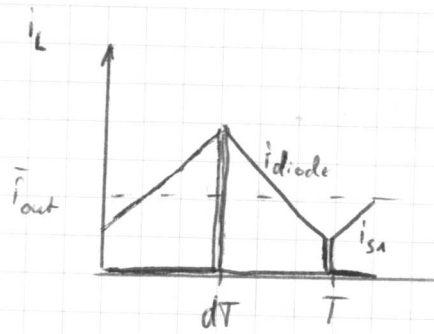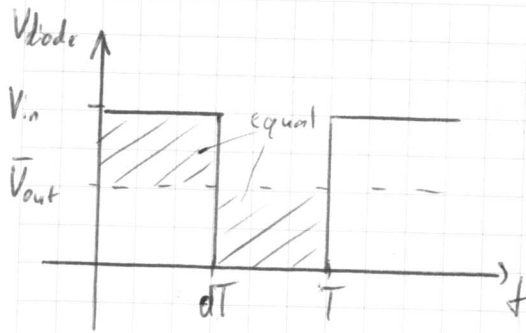1) Continuous Conduction Mode (CCM)

duty cycle d
 $0 < d < 1$
 S_a on D_a off
 $\Rightarrow V_L = V_{in} - V_{out} > 0$
 $\Rightarrow$ current increases
 $V_L = L \cdot \frac{di_{out}}{dt}$
 $dT_s < \frac{1}{f_s} < T_s$
 S_a off D_a on
 $\Rightarrow V_L = -V_{out} < 0$
 $\Rightarrow$ current decreases with $V_L = L \cdot \frac{di_{out}}{dt} < 0$



$$\text{Since } V_L = 0 = dT_s (V_{in} - V_{out}) + (1-d)T_s (-V_{out}) = dT_s V_{in} - T_s V_{out}$$

$$\Rightarrow V_{out} = d V_{in} \quad \bar{P}_{in} = \bar{P}_{out}$$

$$\Rightarrow \bar{I}_n = d \bar{I}_{out}$$

2) Discontinuous Conduction Mode (DCM)

$\rightarrow i_{out} = 0$ during period

$$0 \leq t < dT_s \quad S_1 \text{ on } D \text{ off}$$


$$V_L = V_{in} - V_{out} \Rightarrow \frac{di_{out}}{dt} > 0$$

$$dT_s \leq t < (d+\epsilon)T_s \quad S_1 \text{ off } D \text{ on}$$

$$V_L = -V_{out} \Rightarrow \frac{di_{out}}{dt} < 0$$

$$(d+\epsilon)T_s \leq t < T_s \quad S_1 \text{ off } D \text{ off}$$
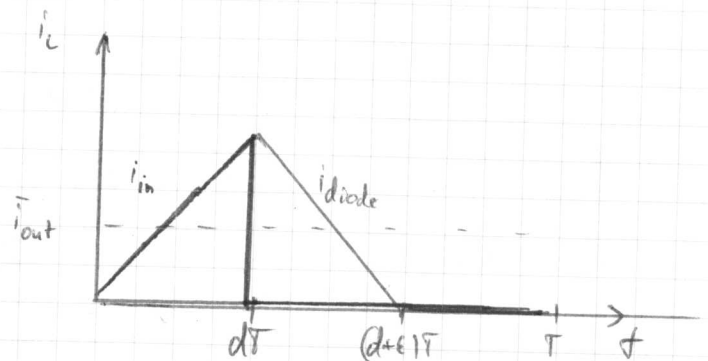
$$V_L = 0V \quad V_{diode} = V_{out} \quad V_{S1} = V_{in} - V_{out} \quad i_L = 0A!$$





Calculation of DCM

$$(V_{in} - V_{out}) dT_s = V_{out} \cdot \epsilon T_s \Rightarrow \frac{V_{out}}{V_{in}} = \frac{d}{d+\epsilon} \quad \text{for DCM}$$

$$\bar{I}_{out} = \bar{i}_L = \frac{1}{2} \underbrace{(d+\epsilon)}_{< 1}$$

$$\text{with } \hat{i} = V_{out} \frac{\epsilon T_s}{L} \Rightarrow \bar{I}_{out} = \frac{V_{out} \cdot \epsilon \cdot T_s}{2L} (d+\epsilon) = \frac{V_{in}}{2L} \cdot T \cdot d \cdot \epsilon$$

$\Rightarrow \epsilon$ is load dependent

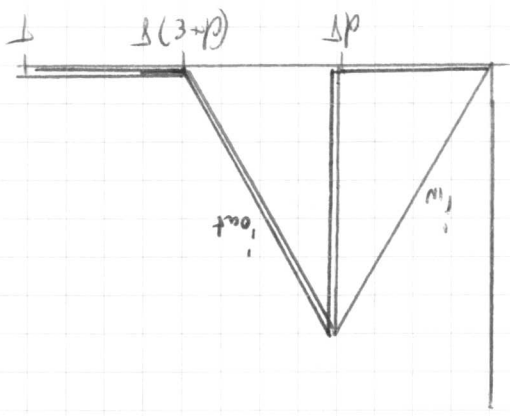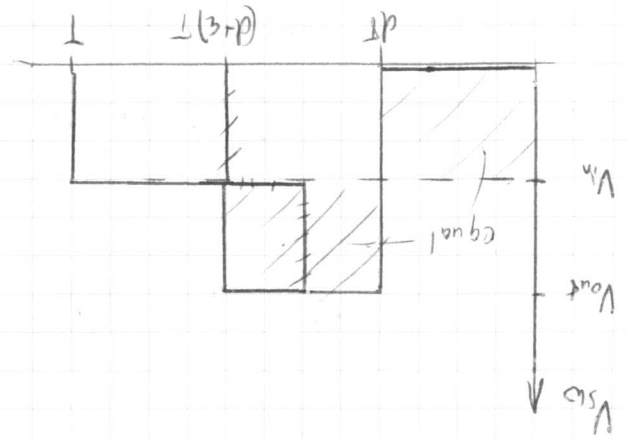

$$dT \leq t \leq T$$



$$dT \leq t \leq (1-d)T$$

$$0 < t < dT$$

$$\begin{aligned} \bar{P}_{in} &= \bar{P}_{out} \\ \bar{P}_{in} &= \frac{1-d}{T} V_{in} \\ \bar{P}_{out} &= (1-d) \bar{P}_{in} \end{aligned}$$

$$d V_{in} + (1-d) V_{in} - V_{out} = 0$$

Since $V_L = 0$ in steady state

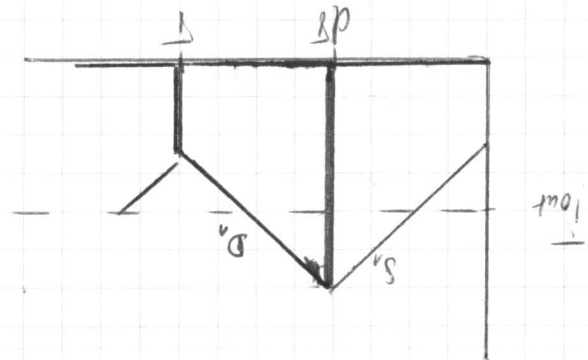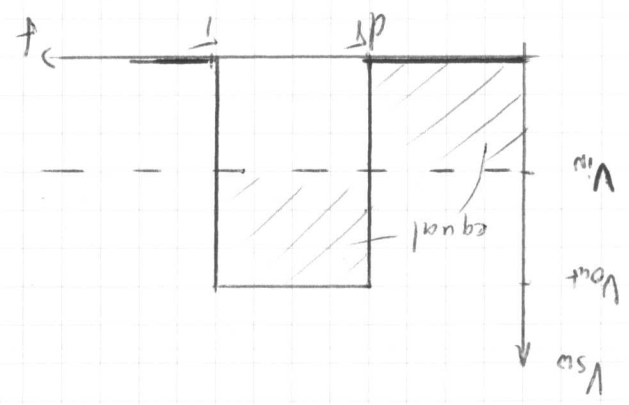

$$\Rightarrow V_L = V_{in} - V_{out} < 0 \Rightarrow \frac{dV_L}{dt} < 0$$

$$s_r \text{ off } D \text{ on}$$


$$V_L = V_{in} > 0 \Rightarrow \frac{dV_L}{dt} > 0$$

$$s_r \text{ on } D \text{ off}$$

$$dT \leq t \leq T$$

$$0 \leq t < dT$$

1) CCM

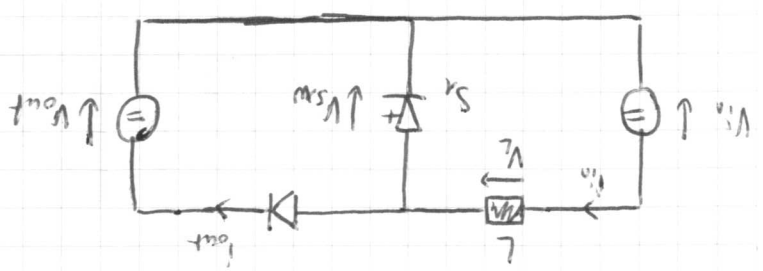

Boost Converter

always: $V_{in} < V_{out}$

no losses

$$V_{in} dT_s = (V_{out} - V_{in}) \varepsilon T_s$$

$$\Rightarrow \frac{V_{out}}{V_{in}} = \frac{d + \varepsilon}{\varepsilon}$$

$$\bar{I}_{out} = \frac{\hat{I}_{out}}{2} \varepsilon$$

$$\text{with } \hat{I}_{out} = \frac{V_{in} d \cdot T_s}{L} \Rightarrow \bar{I}_{out} = \frac{V_{in} \cdot d \cdot \varepsilon \cdot T}{2 \cdot L}$$

Ideal Inductor Model

• Magnetic flux density B

• " field strength H

$$B = \mu \cdot H$$

• permeability $\mu = \mu_r \cdot \mu_0$

• magnetic flux ϕ

$$\phi = \iint_{A_{\perp}} B \cdot dA$$

$$u_L = -N \cdot \frac{d\phi}{dt} = L \cdot \frac{di}{dt}$$

$$W = \frac{1}{2} \cdot L \cdot I^2$$

• Number of turns N

• magnetic path length l_m

• cross sectional area of the core A_c

• length of airgap l_{airgap}

$$L = \frac{B \cdot A_c \cdot N}{i} \quad \text{with } (*)$$

with $\mu_{air} \approx 1$, $\mu_{core} \gg 1$

$$\Rightarrow L = \underbrace{\frac{A_c \cdot \mu_0}{l_{airgap}}}_{A_L} \cdot N^2$$

A_L = characteristic core parameter

$$i = \frac{B \cdot l_{airgap}}{N \cdot \mu_0}$$

Design approach

(*) implies that B_{max} is reached for I_{max}

Always $B < B_{sat}$

$$I_{ken} = \frac{N \cdot A_{cu}}{A_w}$$

According Ex. 5.1

$L = 8 \text{ mH}$ $I_{\text{max}} = 700 \text{ mA}$ $B_{\text{max}} = 300 \text{ mT}$ $A_c = 146 \text{ mm}^2$ $A_0 = 15 \text{ mm}^2$

$k_{cu} = 0.866$ $D = 0.95 \text{ mm}$

$A_c \text{ (mm}^2\text{)}$	$A_0 \text{ (mm}^2\text{)}$
5050	1
630	2
400	3
315	4

③ $N = 141$ ④ $N = 159$

② $N = 40$ ③ $N = 113$

$L \approx A_c \cdot N^2$

$N = \sqrt{\frac{L}{A_c}}$

$= 147.01$

$N_{\text{max}} = \frac{A_{cu} \cdot k_{cu}}{A_0 \cdot k_{cu}} = \frac{15 \text{ mm}^2 \cdot 0.866}{(0.95 \text{ mm})^2 \cdot \pi}$

Number ④ is not possible because of B_{max}

Ex. 5.8 $I_{\text{max}} \approx \frac{B_{\text{max}} \cdot k_{\text{airgap}} \cdot A_c}{N \cdot \mu_0}$ with $A_c = \frac{A_c \cdot \mu_0}{k_{\text{airgap}}}$


$\approx \frac{B_{\text{max}} \cdot k_{\text{airgap}} \cdot A_c}{N \cdot \mu_0} = \frac{B_{\text{max}} \cdot A_c}{N \cdot \mu_0}$

① $I_{\text{max}} = \frac{300 \text{ mT} \cdot 146 \text{ mm}^2}{40 \cdot 5050 \text{ mm}^2} = 217 \text{ mA}$


② $I_{\text{max}} = \frac{300 \text{ mT} \cdot 146 \text{ mm}^2}{113 \cdot 630 \text{ mm}^2} = 615 \text{ mA}$

③ $I_{\text{max}} = \frac{300 \text{ mT} \cdot 146 \text{ mm}^2}{141 \cdot 400 \text{ mm}^2} \approx 777 \text{ mA} \Rightarrow$ ③

Exercice F) F.1) S closed

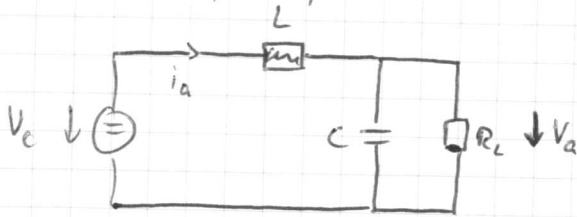

S open

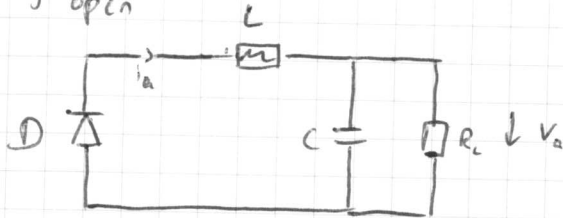

F.2) ~~steady-state~~ $\bar{I}_a = \frac{V_a}{R_L}$

F.2) S closed $\frac{di_a}{dt} = \frac{V_c - V_a}{L}$

S open $\frac{di_a}{dt} = -\frac{V_a}{L}$


F.3) steady state $\bar{I}_a = \frac{V_a}{R_L}$

$I_{a,min} > 0$ (CH)

$I_{a,min} = \frac{V_a}{R_L} - \left(\frac{1}{2} \frac{di_a}{dt} \cdot dT \right)$

with $d = \frac{V_a}{V_c}$

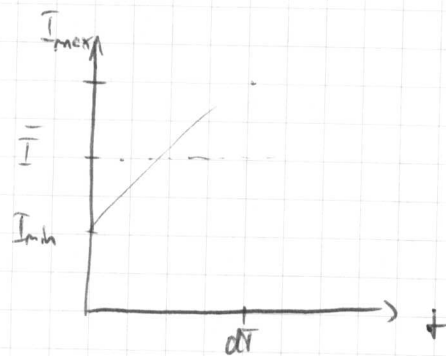$\Rightarrow I_{a,min} = \frac{V_a}{R_L} - \frac{1}{2} \left(\frac{V_c - V_a}{L} \cdot \frac{V_a}{V_c} \cdot dT \right)$



F.4(I) $V_c \rightarrow L$; $V_c \rightarrow R$

(II) $V_c \rightarrow L$; $V_c \rightarrow R$; $V_c \rightarrow C$

(III) $L \rightarrow C$; $L \rightarrow R$

(IV) $L \rightarrow R$; $C \rightarrow R$

F.5) $P = W_{tot} \cdot \frac{1}{T}$

F.6) $P_{out} = \text{const}$ $\eta = 50\%$

$P_{tot} = P_{loss} + \frac{V_a^2}{R_L}$

$P_{loss} = \frac{V_a^2}{R_c}$

$W_{tot} \cdot \frac{1}{T} = P_{loss} \approx \frac{V_a^2}{R_L}$

$\Leftrightarrow \eta_{50\%} = \frac{V_a^2}{R_c} \cdot \frac{1}{W_{tot}}$

F.7) MOSFET conduction losses

Inductance copper losses

Hysteresis "

Power Electronics


Half-Bridge Inverter

Generation of $v_{pu}(t)$ by switching S_1 & S_2 according to modulation scheme.

Target: $v_{pu}(t)$ identical with $v_{load}^*(t)$ (AC or DC)


regardless of $i_{out}(t)$

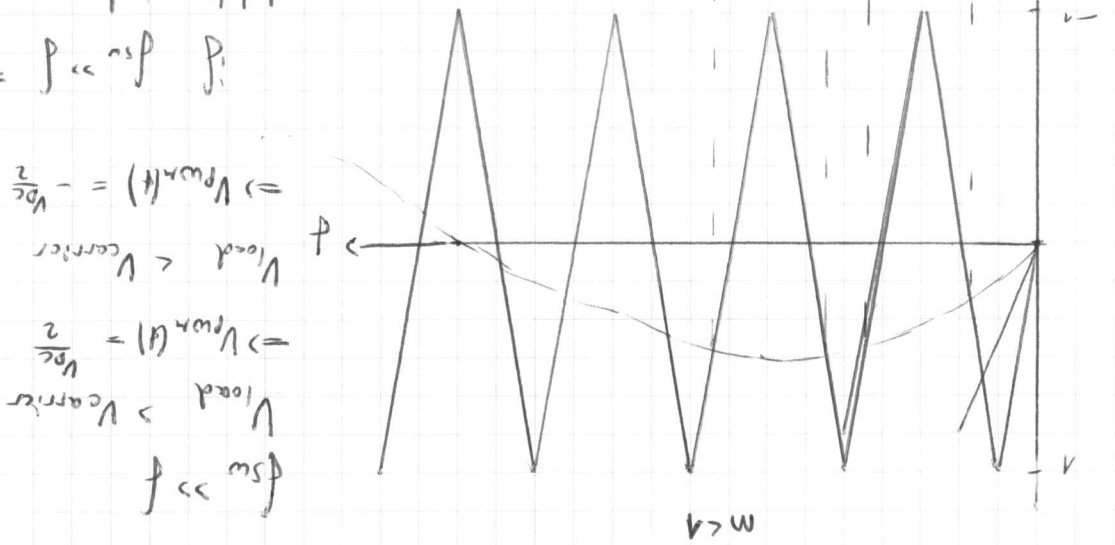S_1 on S_2 off $\Rightarrow v_{pu}(t) = \frac{V_{dc}}{2}$
 S_1 off S_2 on $\Rightarrow v_{pu}(t) = -\frac{V_{dc}}{2}$



$f_{sw} \gg f$
 $V_{load} > V_{carrier} \Rightarrow v_{pu}(t) = \frac{V_{dc}}{2}$
 $V_{load} < V_{carrier} \Rightarrow v_{pu}(t) = -\frac{V_{dc}}{2}$

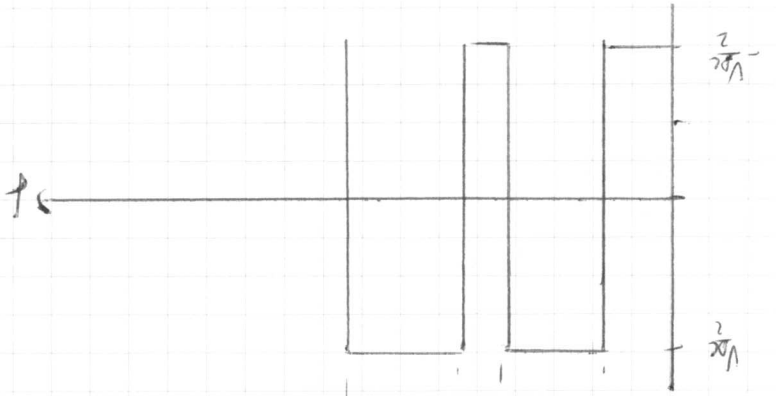$f_{sw} \gg f \Rightarrow \bar{v}_{pu} = v_{load}^*$
 modulation index $m = \frac{\bar{v}_{pu}}{\frac{V_{dc}}{2}}$



- Overmodulation: $m > 1$ (see Lecture Notes)
- Overmodulation: square wave operation
- $m < 1$

} schemes in LE


easy to filter

difficult to filter


$$\hat{v}_{PWM}(t) = \frac{2}{\pi} \int_0^{\pi} \frac{V_{DC}}{2} \sin y dy$$

$$= \frac{4}{\pi} \cdot \frac{V_{DC}}{2}$$
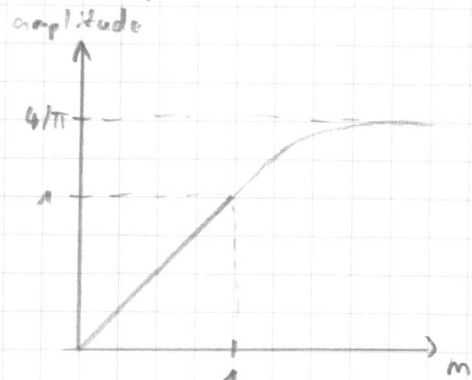
$$\frac{\frac{4}{\pi} \cdot \frac{V_{DC}}{2}}{\frac{V_{DC}}{2}} = \frac{4}{\pi} \approx 1.3$$



Space Vector Modulation

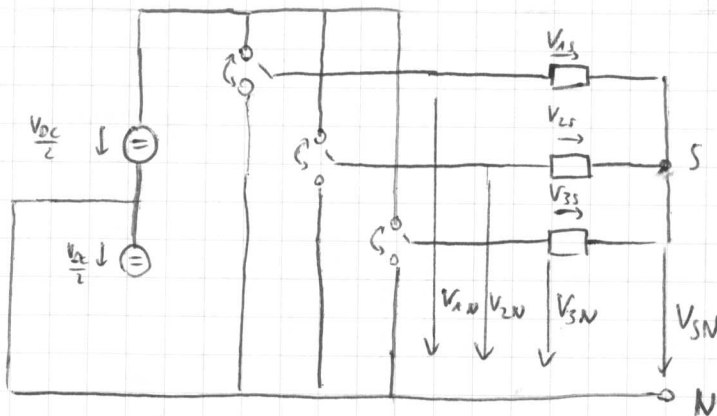

Following voltages have to be generated

$$v_{1s}^* = \hat{v} \cdot \cos(\omega t)$$

→ symmetric system

$$v_{2s}^* = \hat{v} \cdot \cos(\omega t - \frac{2\pi}{3})$$

→ transformation into two axis system

$$v_{3s}^* = \hat{v} \cdot \cos(\omega t - \frac{4\pi}{3})$$

$$\underline{\text{Def:}} \quad \underline{v}(t) = \frac{2}{3} (V_{1s}(t) + \underline{a} V_{2s}(t) + \underline{a}^2 V_{3s}(t))$$

$$\underline{a} = e^{j\frac{2\pi}{3}}$$

$$e^{j\varphi} = \cos(\varphi) + j \sin(\varphi)$$

$$V_d(t) + j V_q(t)$$



$$\Rightarrow \begin{pmatrix} V_d \\ V_q \end{pmatrix} = \frac{2}{3} \begin{pmatrix} 1 & -\frac{1}{2} & -\frac{1}{2} \\ 0 & \frac{\sqrt{3}}{2} & -\frac{\sqrt{3}}{2} \end{pmatrix} \begin{pmatrix} V_{1s} \\ V_{2s} \\ V_{3s} \end{pmatrix} = \begin{pmatrix} \frac{2}{3} & -\frac{1}{3} & -\frac{1}{3} \\ 0 & \frac{1}{\sqrt{3}} & -\frac{1}{\sqrt{3}} \end{pmatrix} \begin{pmatrix} V_{1s} \\ V_{2s} \\ V_{3s} \end{pmatrix}$$

$$V_{1N}, V_{2N}, V_{3N} = \begin{cases} V_{DC}/2 \\ -V_{DC}/2 \end{cases}$$

$$\Rightarrow 2^3 = 8 \text{ states}$$


6 active
2 zero

State Vector V_n

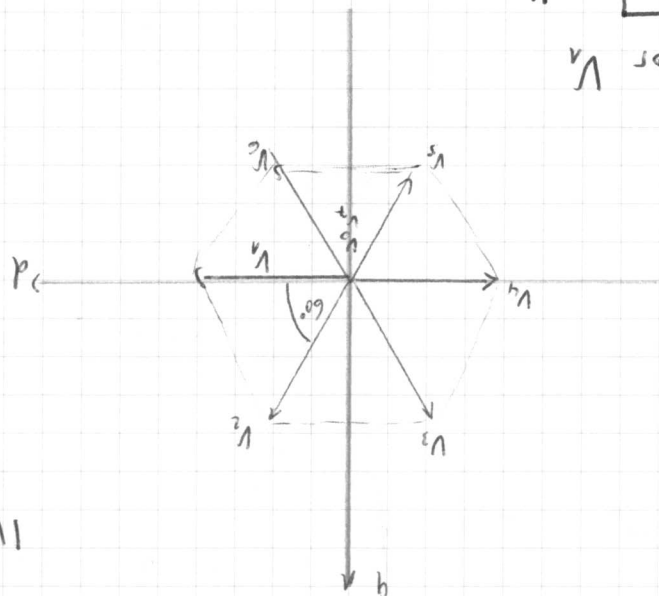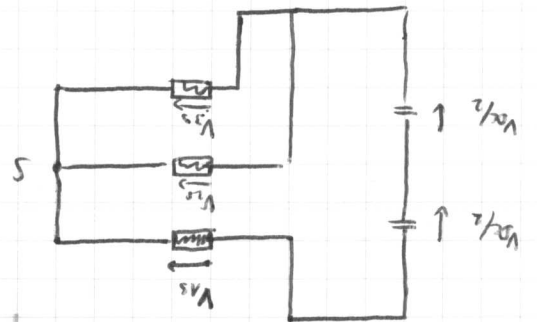

$$|V| = \frac{2}{3} V_{DC}$$
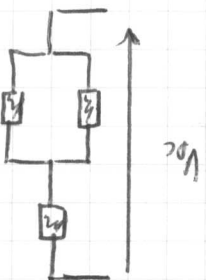
$$\frac{V_{n1}}{V_{DC}} + \frac{V_{n2}}{V_{DC}} + \frac{V_{n3}}{V_{DC}} = -\frac{1}{3}$$



$$\begin{pmatrix} V_d \\ V_q \end{pmatrix} = \frac{2}{3} \begin{pmatrix} 1 & -\frac{1}{2} & -\frac{1}{2} \\ 0 & \frac{\sqrt{3}}{2} & -\frac{\sqrt{3}}{2} \end{pmatrix} \begin{pmatrix} \frac{2}{3} V_{DC} \\ -\frac{1}{3} V_{DC} \\ -\frac{1}{3} V_{DC} \end{pmatrix} = \begin{pmatrix} \frac{2}{3} V_{DC} \\ 0 \end{pmatrix}$$

$\Rightarrow$ Radius of inner circle gives the maximum amplitude

$$|V_{max}| = \sqrt{\left(\frac{2}{3} V_{DC}\right)^2 - \left(\frac{1}{3} V_{DC}\right)^2} = \frac{1}{\sqrt{3}} V_{DC} = 0.577 V_{DC}$$

$\Rightarrow$ same triangle modulation

$$|V_{max}| = \frac{V_{DC}}{2} \quad (\text{without zero-sequence})$$

Exercise K K.1) I, II, III, ~~IV~~

$$K.2) m \leq 1 = \frac{V_{A0}}{\frac{V_{DC}}{2}}$$

$$\Rightarrow V_{DC, \min} = \sqrt{2} \cdot 2 \cdot V_{A0} = 650.53 \text{ V}$$

$$\Rightarrow V_{bat} = \frac{V_{DC}}{30} = 21.68 \text{ V}$$


K.3) Harmonics content of the output

$$K.4) V_{DC, \min} = \sqrt{3} \cdot \sqrt{2} \cdot 230 \text{ V} = 563.38 \text{ V}$$

$$\Rightarrow V_{bat} = \frac{V_{DC, \min}}{30} = 18.78 \text{ V}$$

 $m = 1 \Rightarrow$ vector v^+ is on the inner circle

$$K.5) \varphi^+ = 30^\circ \quad |V^+| = \sqrt{2} \cdot 230 \text{ V} \quad |V_1| = |V_2| = 720 \text{ V} \cdot \frac{2}{3} \quad f_s = \frac{1}{T_s} = 5 \text{ kHz}$$

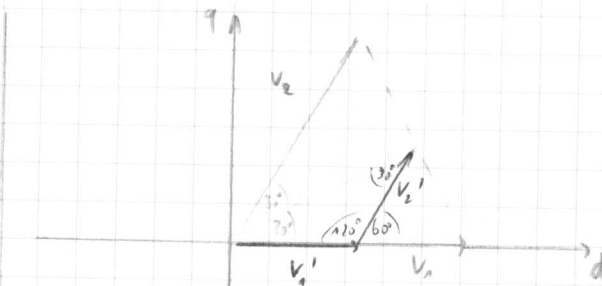Projection of V^+ on V_1 & V_2 $\Rightarrow$ law of sine

$$\frac{a}{\sin \alpha} = \frac{b}{\sin \beta}$$

$$\frac{V^+}{\sin 120^\circ} = \frac{V_2'}{\sin 30^\circ} \Rightarrow V_2' = V^+ \frac{\sin 30^\circ}{\sin 120^\circ} = 187.79 \text{ V}$$

$$\frac{V^+}{\sin 120^\circ} = \frac{V_1'}{\sin 30^\circ} \Rightarrow V_1' = V^+ \frac{\sin 30^\circ}{\sin 120^\circ} = 187.79 \text{ V}$$

$$\text{Duty cycle} \quad T_1 = \frac{V_1'}{V_1} \cdot \frac{T_s}{2} = \frac{187.79 \text{ V}}{\frac{2}{3} 720 \text{ V}} \cdot \frac{200 \mu\text{s}}{2} = 39.1 \mu\text{s}$$

$$T_2 = \frac{V_2'}{V_2} \cdot \frac{T_s}{2} = \dots = 39.1 \mu\text{s}$$

$$\frac{T_s}{2} = T_1 + T_2 + T_0 + T_T$$

$$\Rightarrow T_T + T_0 = 21.8 \mu\text{s} \Rightarrow T_0 = T_T = 10.9 \mu\text{s}$$